

Circuit fits you in a specific band when you talk in a phone. A frequency spectrum will be allocated. All is done by electric circuit.

→ Remote generate unlicensed frequency.


$\text{SNR} \rightarrow \text{Signal Noise Ratio}$

Shannon Capacity


$$C = B \ln(1 + \text{SNR})$$

Bandwidth

Bits/sec

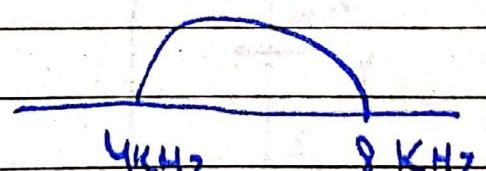


$$\text{Bandwidth} = 4 \text{ kHz}$$

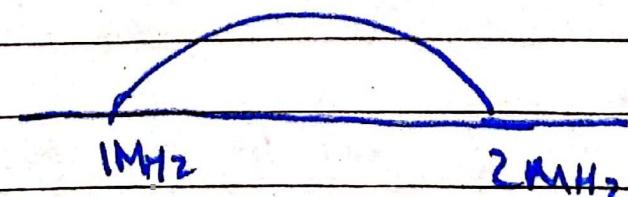

$$B_s = 1 \text{ MHz}$$

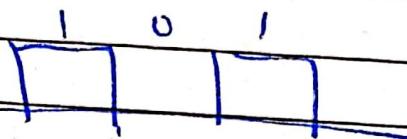→ Filter → Accepts one particular channel frequency and rejects all other.




$\rightarrow$  Frequency Shifting

→ Voltage and current

$$V = \frac{d\omega}{dq} \rightarrow \text{rate of change of expanded energy per unit charge}$$

$$I = \frac{dq}{dt}$$

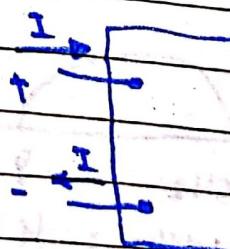

Date: 1/1

Day M T W T F S

$$I=0 \quad t < 0$$

$$tI = 20 e^{-5000t}$$

$$q = ?$$

$$\frac{dq}{dt} = 20 e^{-5000t}$$

$$\int dq = \int 20 e^{-5000t} dt$$

$$q = 20 \int_0^{\infty} e^{-5000t} dt$$

$$= 20 \left[ \frac{e^{-5000t}}{-5000} \right]_0^{\infty}$$

$$q = \frac{1}{\alpha^2} - \left( \frac{1}{\alpha} - \frac{1}{\alpha^2} \right) e^{-\alpha t} \cos$$

$$\alpha = 0.0369 \text{ sec}^{-1}$$

$$q = \frac{1}{\alpha^2} - \left( \frac{\alpha^2 - 1}{\alpha^2} \right) e^{-\alpha t}$$

$$\frac{dq}{dt} = \frac{d}{dt} \left( \frac{1}{\alpha} e^{-\alpha t} - \frac{e^{-\alpha t}}{\alpha^2} \right)$$

→ The output of a circuit may be non-electrical. So we also study other parameters of a circuit i.e. power and energy.


$$P = \frac{dW}{dt}$$

$$S(t)$$

$$\text{Energy of signal} = \int_{-\infty}^{\infty} S^2(t) dt$$

$$\text{Power } P = \frac{1}{T} \int_{-T/2}^{T/2} S^2(t) dt$$

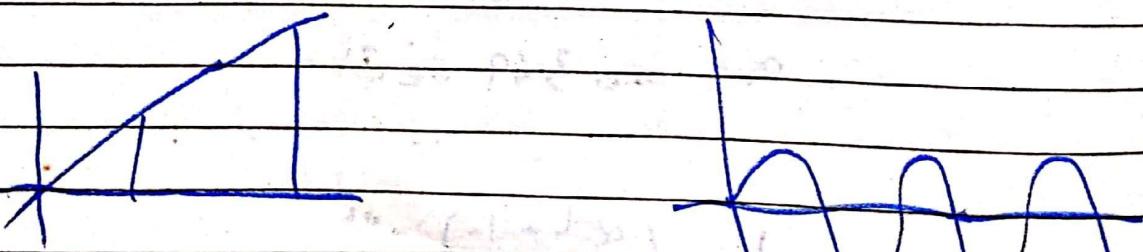→ Signal can be  Energy Signal  
Power  $P$



Average is  
not same

→ Energy is infinite


Date: 11/11/2023

Page No. 11 P =  $\text{GKV} \times \text{vi}$  Day: MTWTFSS

$$P = \frac{dw}{dt} \times \frac{dv}{dt}$$


$$P = \rho_{\text{av}} V I$$

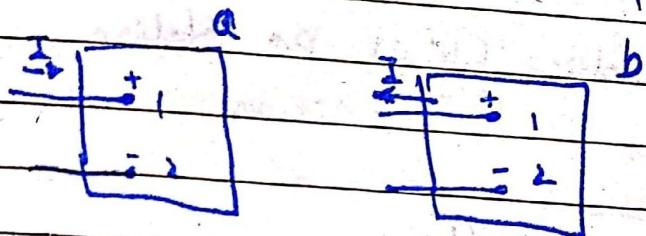Power may be  $\rightarrow$  absorbing  
 Conventional current  $\rightarrow$  releasing/delivering  
 Electronic current



$$P = Vi$$

$$P = v(-i) = -Vi$$

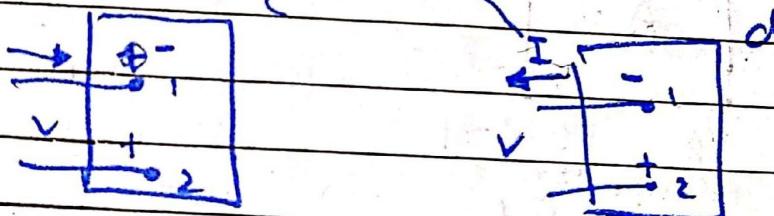

$$P = (-v)i$$

$$P = -Vi$$

$$P = (-v)(-i)$$

$$P = Vi$$

$$\boxed{\begin{aligned} I &= 4A \\ V &= -40 \text{ @V} \end{aligned}}$$

With ref to Box b

$$P = -1 \cdot 40)(4)$$

With ref to Box 9  
the I will be -I


$$P = VI$$

$$P = (40)(-4) = 160 \text{ watt}$$

+ve power  $\rightarrow$  absorbing the power  
-ve power  $\rightarrow$  Extracting it V

Electric Circuit by Nelson  
8<sup>th</sup> Edition

(1)

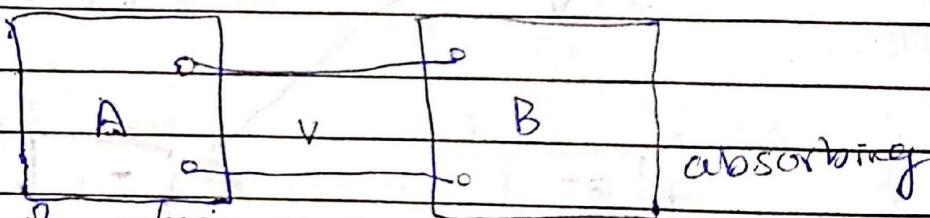

$$P_A = -600 \text{ watts}$$

delivering


$$i = 5 \text{ A}, \quad V = 120 \text{ V}$$

$$i = -8 \text{ A} \quad V = 250 \text{ V}$$

$$i = 16 \text{ A} \quad V = -150 \text{ V}$$

$$i = -10 \text{ A} \quad V = -480 \text{ V}$$

$$i = 30 \text{ A}$$

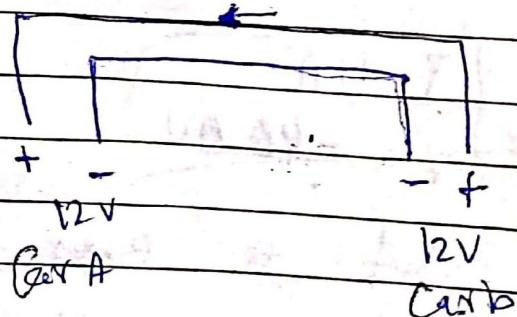

$$P_A = VI = (12)(30) = 360 \text{ watts} \leftarrow \text{absorbing}$$

Date: 11

②

$$360 \times 60$$

$$\begin{array}{r}
 3 \quad 360 \\
 \times \quad 60 \\
 \hline
 21600 \\
 \cancel{\times} \\
 \hline
 21,600
 \end{array}$$

$$P = 360 \text{ Watt}$$

$$dW = 360 \int_0^{60 \text{ sec}} dt$$

=

$$V = e^{-500t} - e^{-1500t} \text{ V}$$

$$i = 30 - 40e^{-500t} + 10e^{-1500t} \text{ mA}$$

$$\underline{P = ?}$$

$$P = \frac{dW}{dq}$$

$$I = \frac{dq}{dt}$$

$$P = (e^{-500t} - e^{-1500t}) (30 - 40e^{-500t} + 10e^{-1500t}) dq = (I \cdot dt)$$


$$\underline{Q =}$$

$$P = 30e^{-500t} - 40e^{-1500t} + 10e$$

Date: / /

Day: MTWTF

(3)

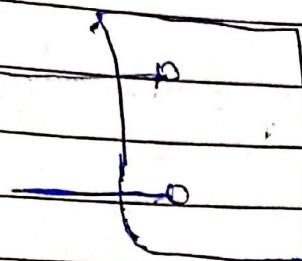

$$V = 0, i = 0 \quad t < 0$$

$$V = 400 e^{-100t} \sin 200t \text{ V} \quad t \geq 0$$

$$I = 5 e^{-100t} \sin 200t \text{ A}$$

$$t = 10^2 \text{ s}$$

$$P = (400 e^{-100t} \sin 200t)(5 e^{-100t} \sin 200t)$$


$$P = 800 e^{-200t} \sin^2 200t$$

$$P = 800 e^{-\frac{200t}{100}} \sin^2 200t \times \frac{100}{100}$$

$$P = 800 e^{-2} \sin^2 2$$


$$P = 0.974 e^{-2}$$

$$P = 6.1318$$

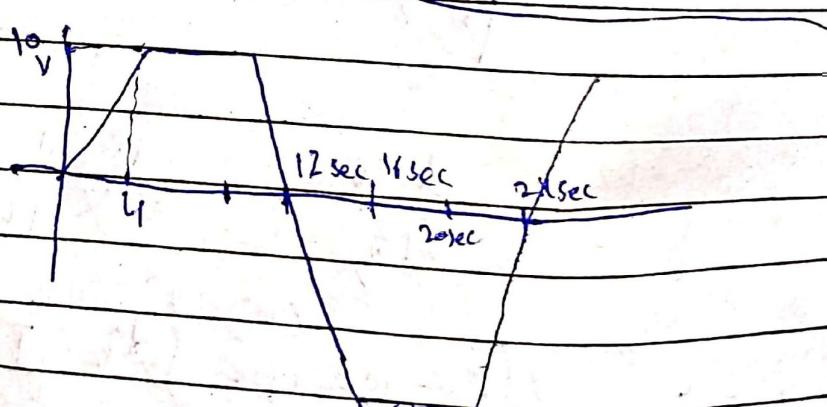

Date: 11/11/11

(4)

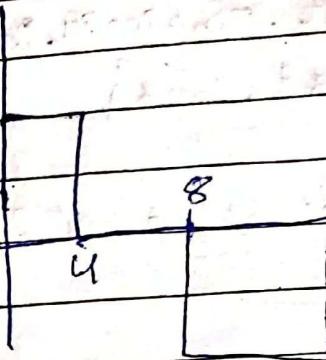

$$V = 75 - 75 e^{-3000t} \text{ volts}$$

$$i = 50 e^{-4000t} \text{ mA}$$

$$P_{\max} = ?$$

$$P = (75 - 75 e^{-3000t})(50 e^{-4000t})$$

$$P = 3750 e^{-1000t} - 3750 e^{-4000t}$$

$$P' = 3750 \cdot e^{-1000t} (-1000) - 3750 (-4000) e^{-4000t}$$

$$P' =$$

$$V = 30 \sin 200\pi t$$

$$I = 20 \cos 200\pi t$$

$$P = \frac{750}{600} \cdot \sin 200\pi t \cdot \cos 200\pi t$$

$$P' = 750 \left\{ \sin 200\pi t, -\sin 200\pi t, 200\pi + (\cos 200\pi t, \cos 200\pi t, 200\pi) \right\}$$

$\Rightarrow 50, 200\pi$

$$P' = 750 \left\{ -\sin^2 200\pi t + \cos^2 200\pi t \right\}$$

$$P = 600 \sin 200\pi t + \cos 200\pi t$$

$$P(t) = 300 \sin 400\pi t$$

$$\omega = 400\pi$$

$$f = ?$$

$$\frac{2\pi f}{2\pi} = \omega$$


$$f = \frac{400\pi}{2\pi} = 200 \text{ Hz}$$

Average value

$$P(0) = 600 \sin 400\pi(0)$$

$$P(0) = 600 \sin(0) \approx 0$$

$$P(5) =$$

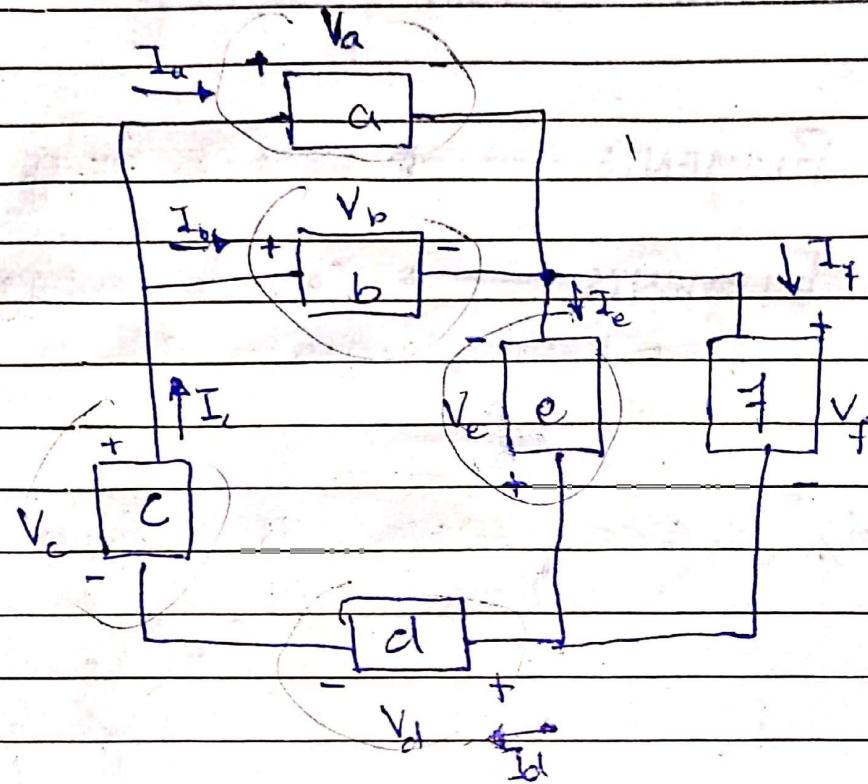

	$V$	$i$	$P$
a	150	0.6	$P = (150)(0.6) = 90 \text{ Watt}$
b	150	-1.4	$P = (150)(-1.4) = -210 \text{ Watt}$
c	100	-0.8	$P = (-i)V = (-0.8)(100) = 80$
d	250	-0.8	$P = (+V)i = (250)(-0.8) = -200$
e	300	-2.0	$P = -iV = -(2)(300) = 600$
f	-300	1.2	$P = iV = 360$

$$\begin{array}{r}
 300 \\
 1.2 \\
 \hline
 600 \\
 300 \\
 \hline
 360
 \end{array}$$

# VOLTAGE AND CURRENT SOURCES :-

**ACTIVE ELEMENTS** → Provide energy to circuit

**PASSIVE ELEMENTS** → Consume energy from circuit  
↳ Resistor, capacitor etc.

→ Ideally Sine wave is from  $+\infty$  to  $-\infty$ .



Ideal Voltage Source

Ideal Current Source

The Source which maintain its voltage whatever is the current flowing.

The Source which maintain its voltage whatever is the current voltage.



→ Two types of active sources

\* Dependant voltage & current sources


\* Independent

Date: 11


Day: MTWTF

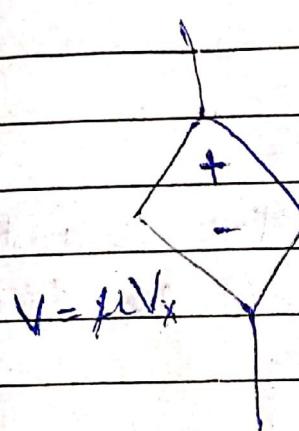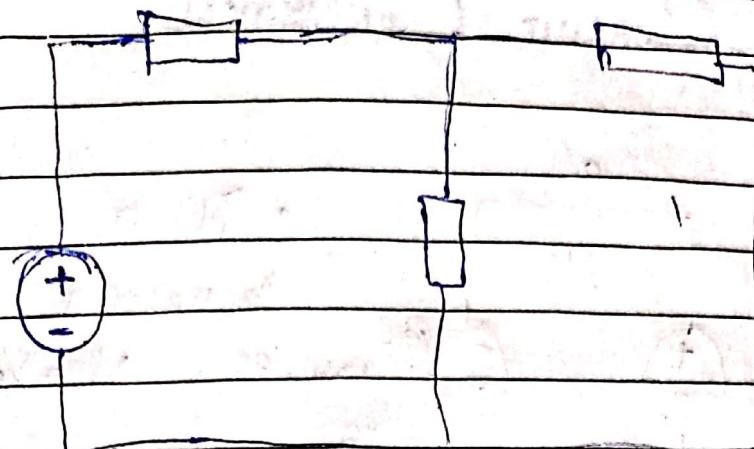

Voltage dependant  
Voltage source

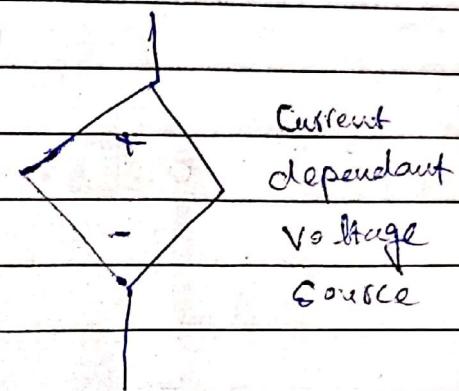

$$i = f(Vx)$$

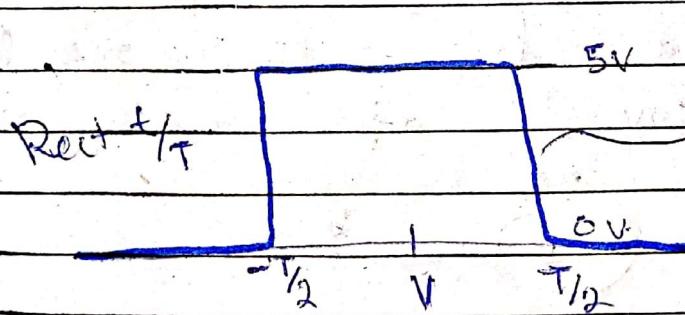


→ Ideally  
drops to zero.




$$i = 2Vx$$

→ These symbols are constant values.

Date: 1/1

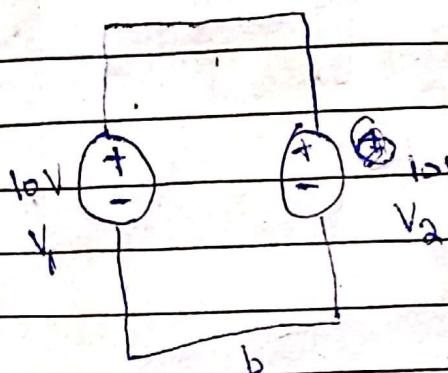
CIRCUIT CONNECTIONS

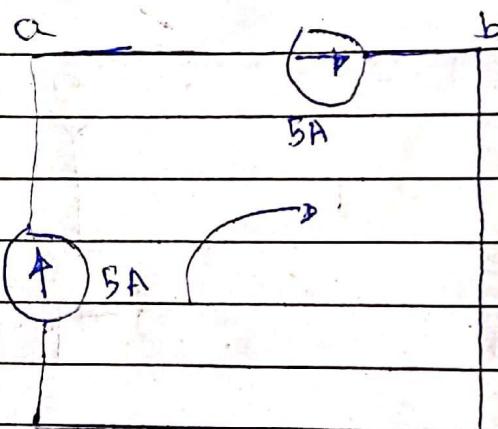• It is a valid connection as long as  $V_1 = V_2$



★ Here current won't be added.

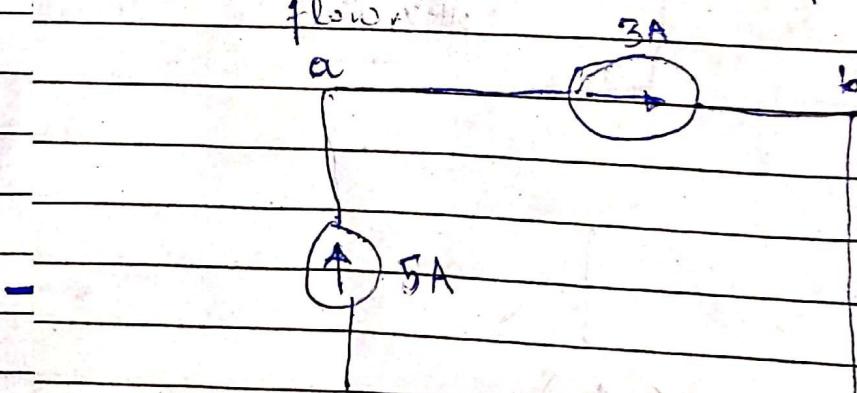★ It is a loop and in one loop same amount of current will flow.



Not valid

Line Elements


↳ Line losses

b/c of these elements.

R, L, C


Date: 1/1/20

Day MTWTF

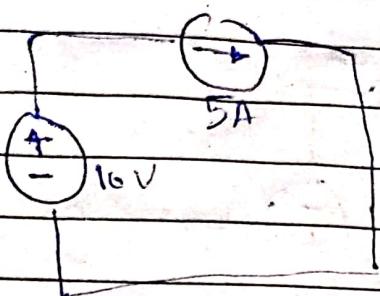

By definition  
It is a valid connection.


### Assessment Problem.

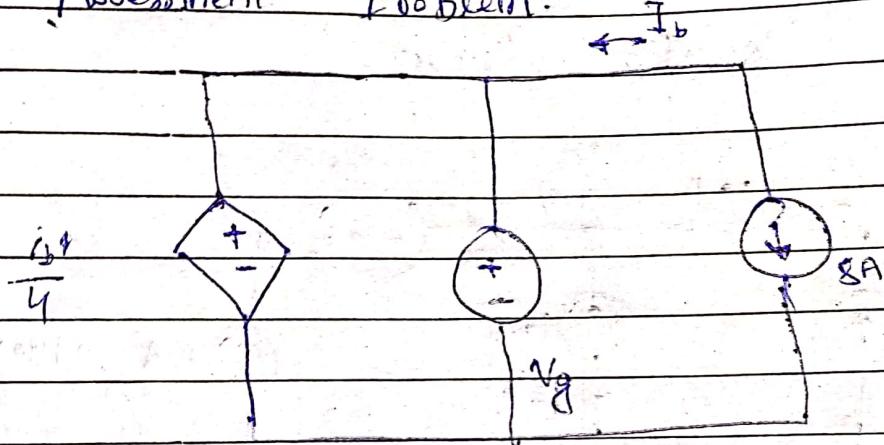

$$V = -\frac{8}{4} = -2 \text{ Volts}$$

$$P = VI = -2 \times 8 = -16 \text{ Watts}$$



$$\therefore V_x = 25$$

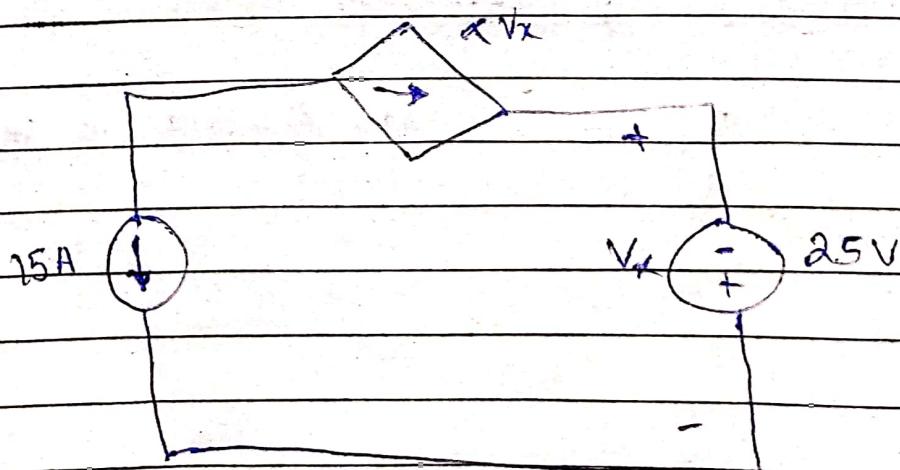

Date: 5 / 4 / 2022

lect #5

Day: MTWTF

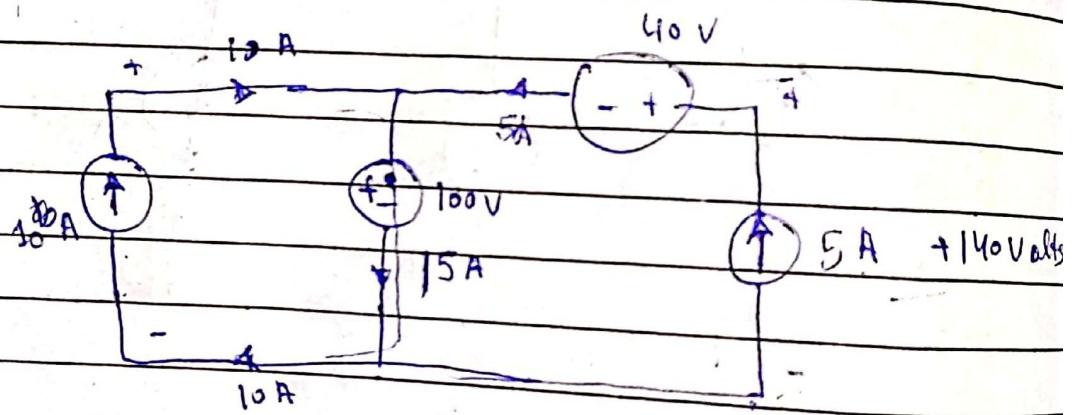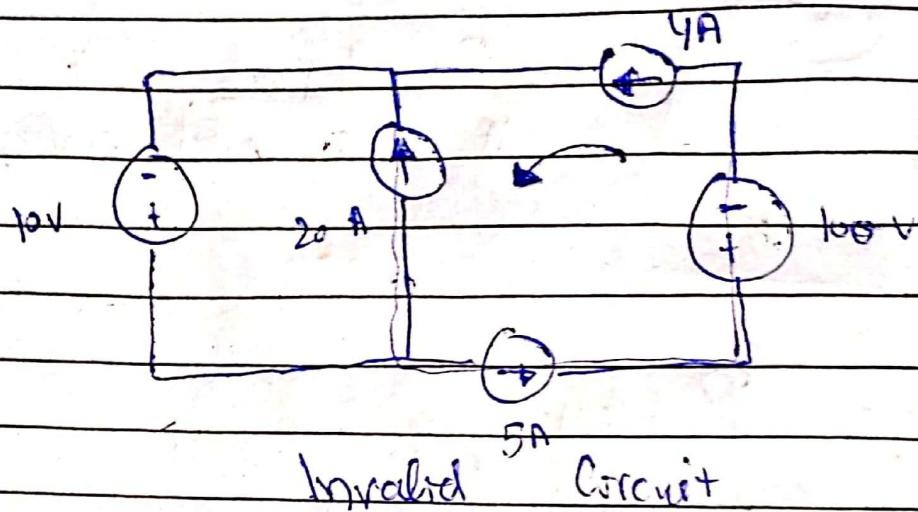



$$P_{10A} = (-10)(100) = -1000 \text{ Watts}$$

$$V = 10$$

$$\begin{aligned} P_{5A} &= -(140)(5) \\ &= -700 \text{ Watts} \end{aligned}$$

$$\begin{aligned} P_{100V} &= V_i = 100 \times 15 = 1500 \text{ Watts} \end{aligned}$$

Date: 1/1

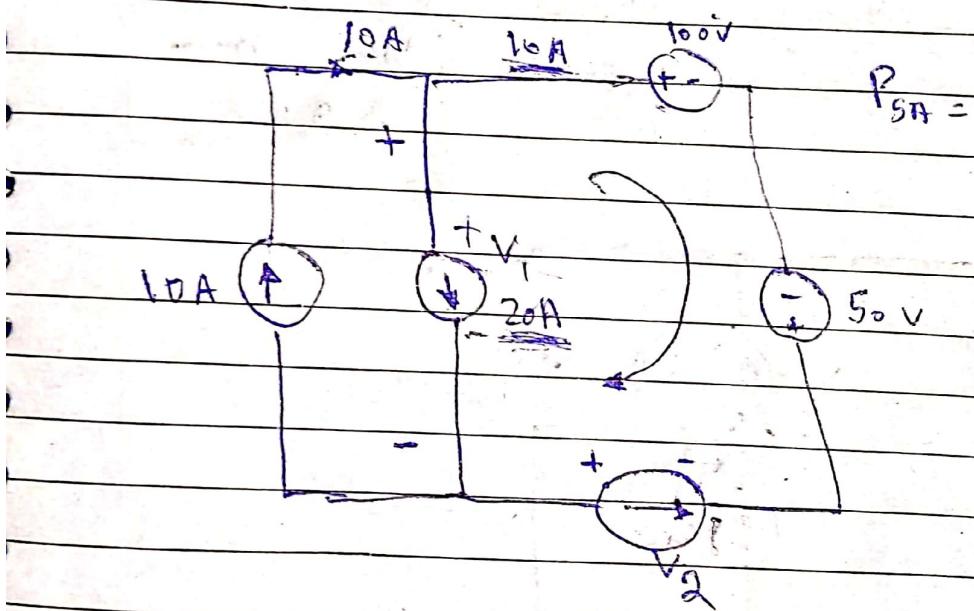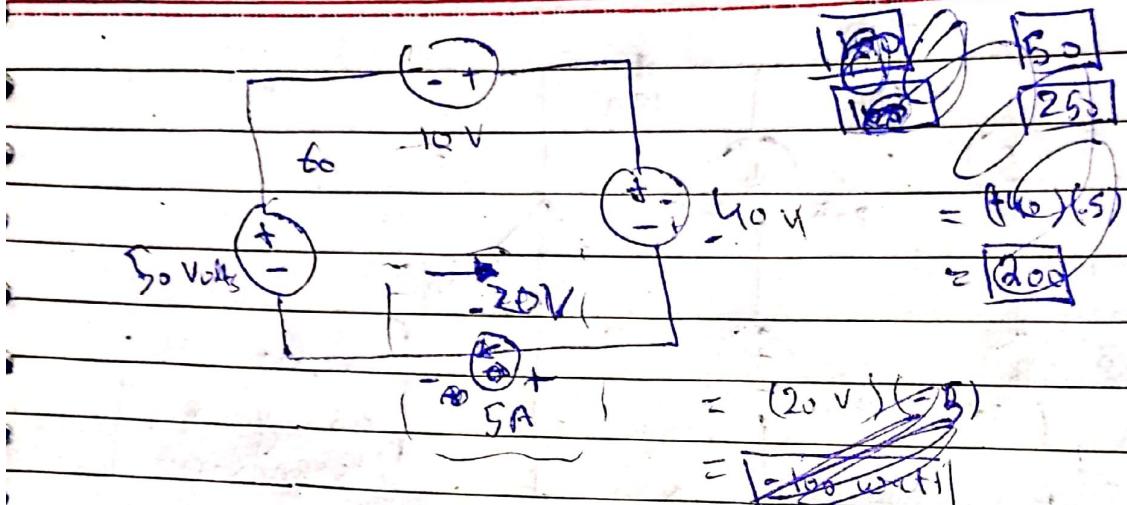


$$\underline{100 \text{ V}} - \underline{50 \text{ V}} = \underline{V_2} - \underline{V_1} = 0$$

$$50 \text{ V} = \underline{V_1} + \underline{V_2}$$


Doesn't have unique solution.  
 Infinite solutions.

Date: / /

Day: MTWTF

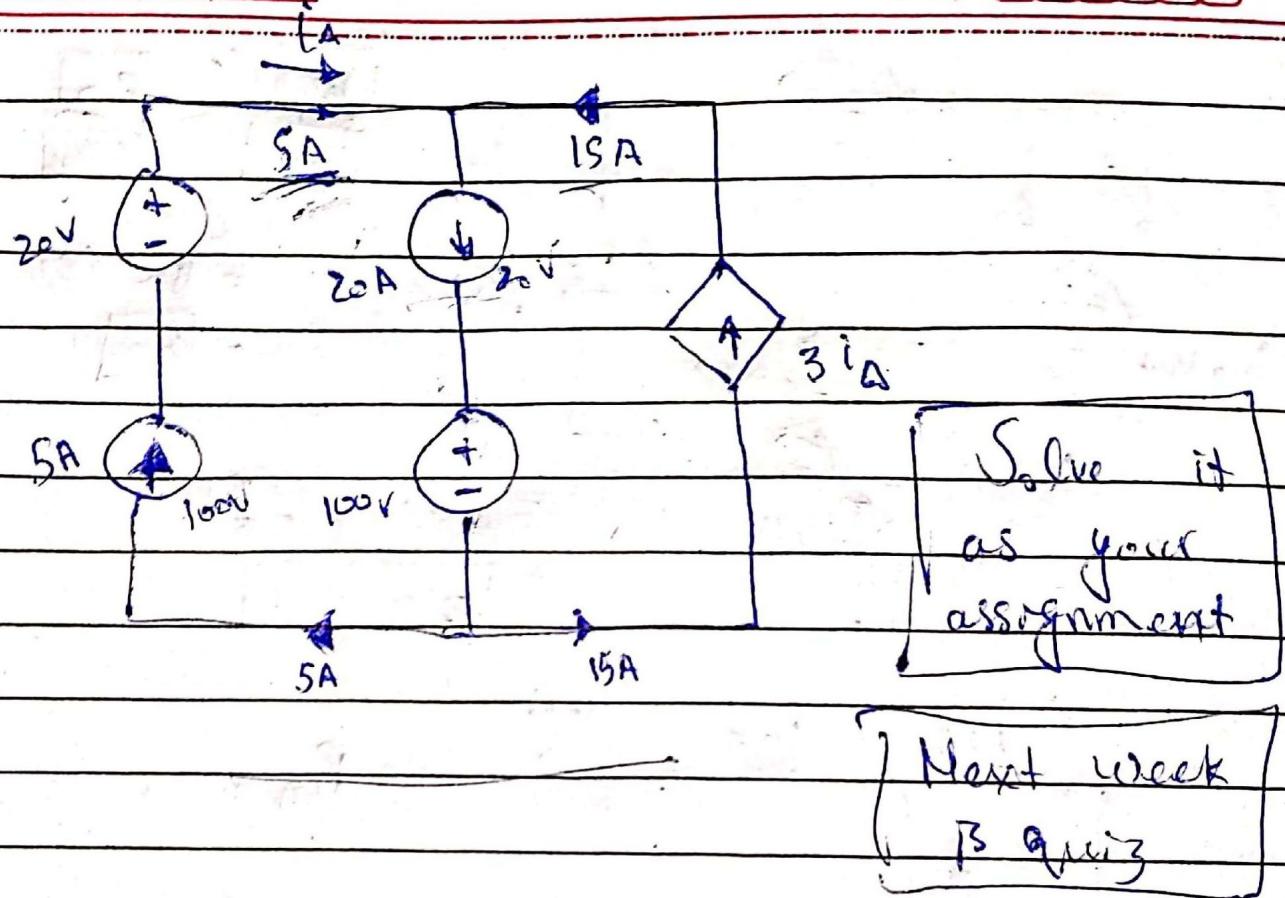

Next week  
B quiz

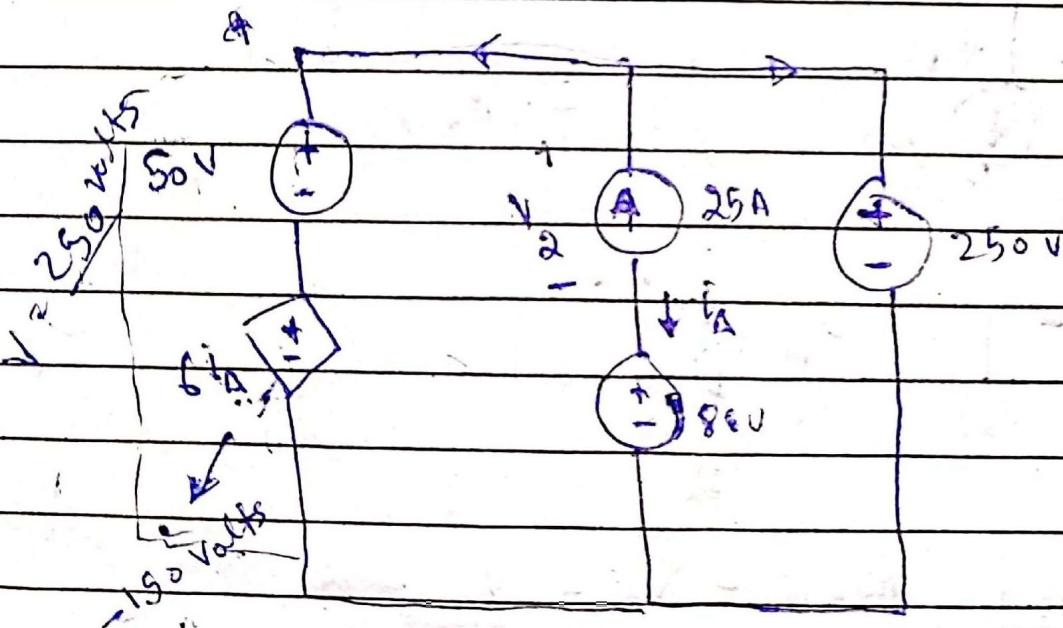

The circuit is invalid