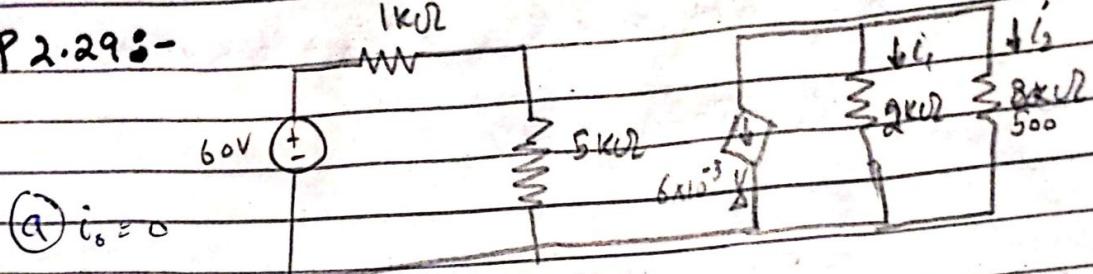


P 2.29 :-



(a) $i_6 = 0$

(b)

$$60 = 6000 i_g$$

$$i_g = 10 \text{ mA}$$

$$V_A = 5000 i_g = 50 \text{ V} \quad 6 \times 10^{-3} V_A = 300 \text{ mA}$$

$$2000 i_1 = 500 i_1 \quad \text{So } i_1 + 4i_1 = -300 \text{ mA}$$

$$\therefore i_1 = -60 \text{ mA}$$

(c) $300 - 60 + i_2 = 0,$

$$\Rightarrow i_2 = -240 \text{ mA}$$

P 2.30 :-

$$50 i_2 + \frac{0.250}{50} + \frac{0.250}{12.5} = 0 \quad i_2 = -0.5 \text{ mA}$$

$$V_1 = 100 i_2 = -5 \text{ mV}$$

$$20 i_1 + \frac{(-0.050)}{25} + (-0.0005) = 0 \quad i_1 = 125 \text{ mA}$$

~~50i₂~~

$$V_g = 10i_1 + 40i_1 = 50i_1$$

$$\therefore V_g = 6.25 \text{ mV}$$

P 2.31 :-

(a) $-50 - 20i_8 + 18i_8 = 0$


$$-18i_8 + 5i_8 + 40i_8 = 0 \quad \text{So } 18i_8 = 45i_8$$

$$\therefore -50 - 20i_8 + 45i_8 = 0, \quad \text{So } i_8 = 2 \text{ A}$$

$$V_o = 40i_8 = 80 \text{ V}$$

$$\therefore i_B = \left[\frac{V_{cc} R_1}{R_1 + R_2} \right] - V_o \\ (1 + \beta) R_E + R_1 R_2 / (R_1 + R_2)$$

P 2.28 :-

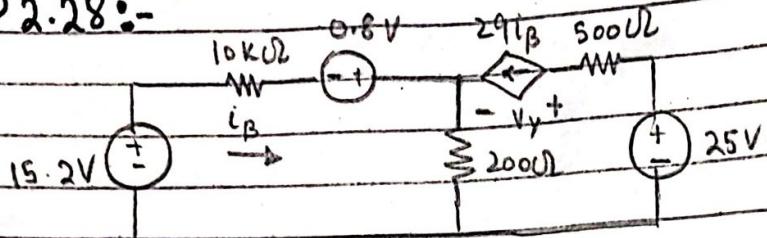

$$i_B + 29i_B = i_{200\Omega} = 30i_B$$

(a) $-15.2V + 10,000i_1 - 0.8V + 6000i_B = 0$

Solving for i_B

$$10,000i_B + 6000i_B = 16V$$

$$i_B = \frac{16}{16,000} = 1mA$$

$$-V_y = 14,500i_B + 25 - 6000i_B = 0$$


$$V_y = 25 - 20,500i_B = 25V - 20,500(10^{-3})$$

$$= 25V - 20.5V = 4.5V$$

(b) The total power generated in the circuit is the sum of the -ve power values in the power table

$$-15.2mW + -0.8mW + -7.5mW = -741mW$$

Q 2.26 :-

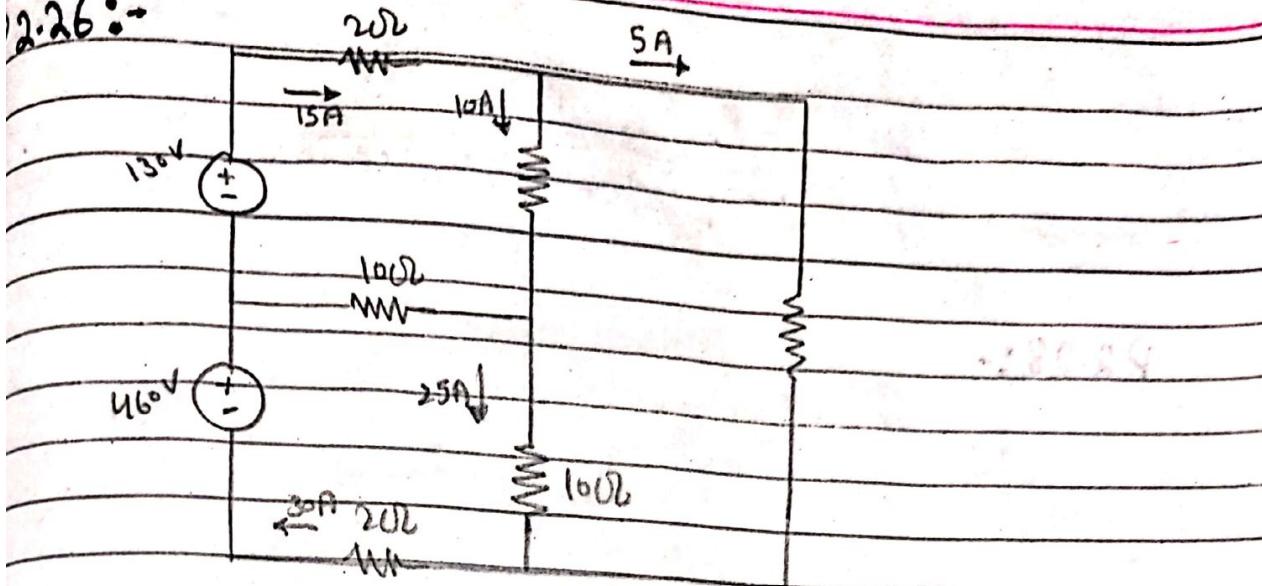

(a)

$$P_{130} = -(130)(15) = -1950 \text{ W}$$

$$P_{460} = -(460)(30) = -13,800 \text{ W}$$

(b)

$$P_{\text{diss}} = (15)^2(2) + (15)^2(10) + (30)^2(2) + (10)^2(25) + (25)^2(10) + (5)^2(100)$$

$$P_{\text{diss}} = 15,750$$

$$P_{\text{del}} = 1950 + 13,800 = 15,750 \text{ W}$$

Q 2.27 :-

$$\text{So } i_E - i_B - i_C = 0$$

$$i_C = \beta i_B$$

$$i_2 = -i_B + i_1$$

$$V_o + i_F R_B - (i_1 - i_B) R_2 = 0$$

$$-i_1 R_1 + V_{cc} - (i_1 - i_B) R_2 = 0$$

$$V_o + i_F R_F + i_B R_2 = \frac{V_{cc} + i_B R_2 R_F}{R_F + R_B}$$

$$P_{5kW} = (5000)(0.06667)^2 = 22.22 \text{ W}$$

$$P_{10kW} = (10,000)(0.03333)^2 = 11.11 \text{ W}$$

$$P_{7.5kW} = (7500)(0.06667)^2 = 33.33 \text{ W}$$


$$P_{15k} = (15,000)(0.03333)^2 = 16.67 \text{ W}$$

$$P_{4kW} = (4000)(0)^2 = 0 \text{ W}$$

(b) $V_{ad} = 5000i_{ab} + 7500 i_{bd} = 5000(0.067) + 7500(0.067)$
 $V_{ad} = 833.33 \text{ V}$

$$P_{cs} = -833.33(0.1) = -83.33 \text{ W}$$

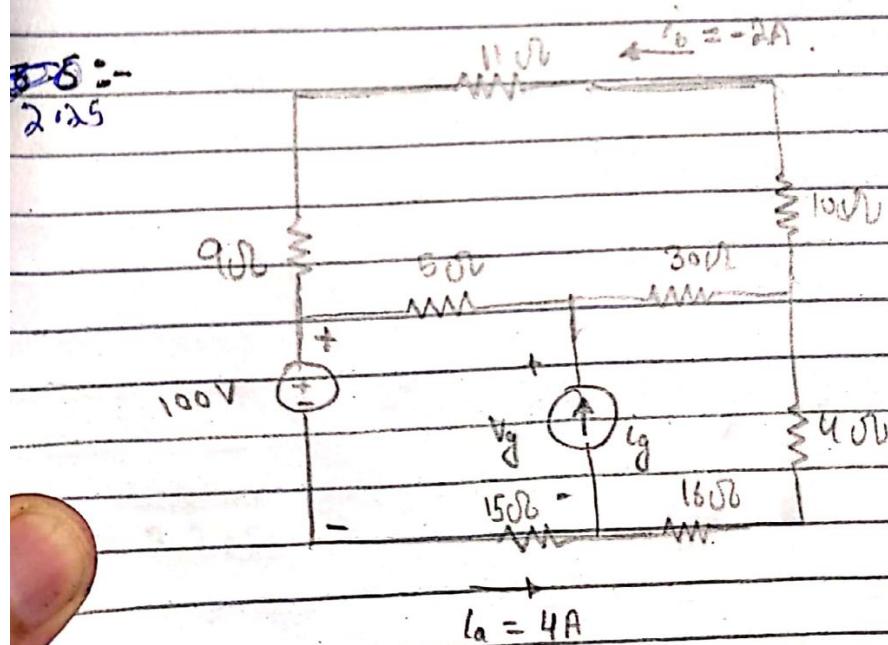(c) $P_{ab} / P_{abc} = 22.22 + 33.33 + 11.11 + 16.67 + 0$
 $I_1 = 83.33 \text{ W}$



$$\text{hence } i_a = V_{ba} / 180 = \frac{180}{180} = 1 \text{ A}$$

$$i_e = i_a + i_c = 1 \text{ A}$$


$$-240 + V_{ab} + V_{bd} = 0$$

$$V_{ab} = 240 - 180 = 60 \text{ V}$$

Using Ohm's law.

$$R = \frac{V_{ab}}{i_e} = \frac{60}{4} = 15 \text{ k}\Omega$$

PROBLEM 2.24 :-

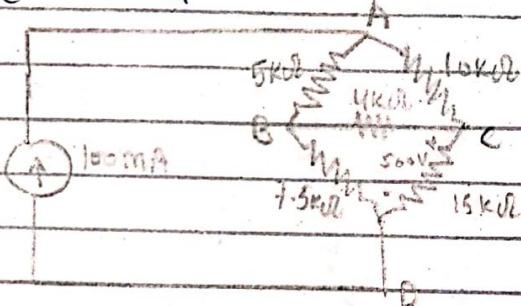

$$i_{col} = \frac{500}{15000} = 33.33 \text{ mA}$$

$$i_{bcl} + i_{col} = 0.1$$

$$\Rightarrow i_{bcl} + 33.33 \times 10^{-3} = 0.1$$

$$i_{bcl} = 66.67 \text{ mA}$$

Using KVL

$$4000 i_{bc} + 500 - 7500 i_{bd} = 0$$

$$\Rightarrow i_{ne} = 0$$

$$i_{ac} = i_{cd} - i_{bc} = 33.33 - 0 = 33.33 \text{ mA}$$

$$0.1 = i_{ab} + i_{ac}$$

$$\Rightarrow i_{ab} = 0.1 - 33.33 = 66.67 \text{ mA}$$

$$\text{hence } i_a = V_{ba} / 180 = \frac{180}{180} = 1 \text{ A}$$

$$i_b = i_a + i_c = [4 \text{ A}]$$


$$-240 + V_{ab} + V_{bd} = 0$$

$$V_{bd} = 240 - 180 = 60 \text{ V}$$

Using Ohm's law.

$$R = \frac{V_{ab}}{i_e} = \frac{60}{4} = [15 \text{ k}\Omega]$$

PROBLEM 2.24 :-

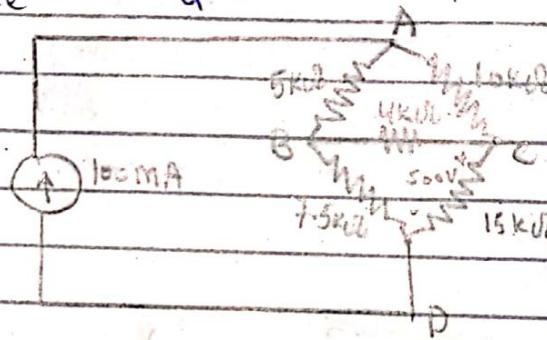

$$i_{cd} = \frac{500}{15000} = 33.33 \text{ mA}$$

$$i_{bcd} + i_{cd} = 0.1$$

$$\Rightarrow i_{bcd} + 33.33 \times 10^{-3} = 0.1$$

$$i_{bcd} = 66.67 \text{ mA}$$

Using KVL

$$4000 i_{bc} + 500 - 7500 i_{bd} = 0$$

$$\Rightarrow i_{bd} = 0$$

$$i_{ac} = i_{cd} - i_{bc}$$

$$i_a = i_d + i_c = 5A$$

$$R = V_d / i_a = 35 / 5 = 7 \Omega$$


(b)

$$P_{dd} = -vi$$

$$P_{dd} = -125(i_a + 3A)$$

$$P_{dd} - 125(5 + 3) = -125(8) = -1000W$$

PROBLEM 2.23 :-

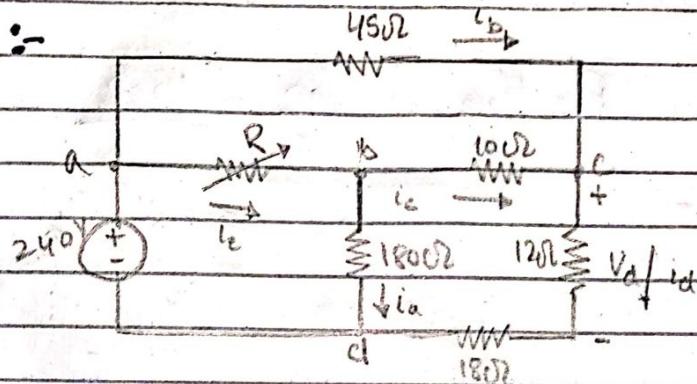

Sol:-

$$i_d = \frac{60}{12} = 5A$$

$$V_{cd} = 60 + 18(3) = 60 + 90 = 150V$$

Using KVL

$$-240 + V_{ac} + V_{cd} = 0$$

$$V_{ac} = 240 - 150$$

$$V_{ac} = 90V$$

$$i_b = \frac{V_{ac}}{45} = \frac{90}{45} = 2A$$

$$\text{Hence } i_c = i_d - i_b = 5 - 2 = 3A$$

$$V_{bd} = 10i_c + V_{cd} = 10(3) + 150 = 180V$$

$$P_{dei} = -Vi$$

$$P_{dei} = -(80)(1+6)$$

$$P_{dei} = -80(7+2)$$


$$P_{dei} = -80(9)$$

$$P_{dei} = -720 \text{ W}$$

Hence verified

PROBLEM 2.22 :-

(a)

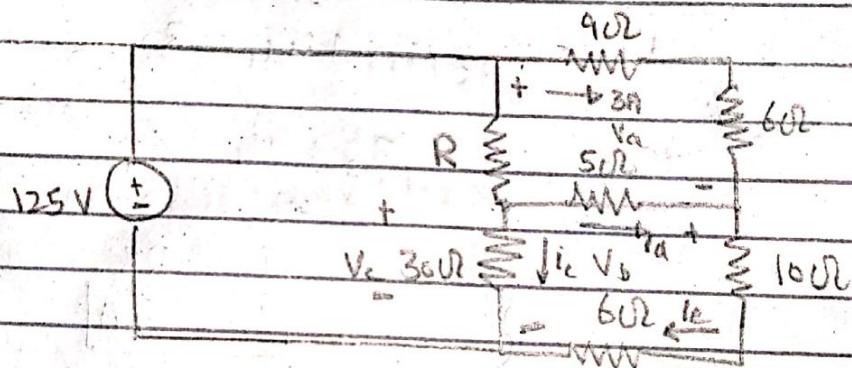

$$V_a = (9+6)(3) = 45 \text{ V}$$

$$-125 + V_a + V_b = 0$$

$$V_b = 125 - V_a = 80 \text{ V}$$

$$I_e = \frac{80}{16} = 5 \text{ A}$$

$$I_d = I_e - 3 = 2 \text{ A}$$

$$V_c = 5i_d + V_b = 10 + 80 = 90 \text{ V}$$

$$i_c = \frac{V_c}{3b} = \frac{90}{30} = 3 \text{ A}$$

$$V_d = 125 - V_c = 125 - 90 = 35 \text{ V}$$

$$-i_2 = -3$$

$$T_L = 3$$

Put in (ii)

$$4(3) + 13i_3 = -40$$

$$12 + 13i_3 = -40$$

$$12 + 40 = 13i_3$$

$$52 = 13i_3$$

$$i_3 = 4 \text{ A}$$

Put in (i)

$$13(4) + 4i_1 = 80$$

$$52 + 4i_1 = 80$$

$$4i_1 = 80 - 52$$

$$4i_1 = 28$$

$$i_1 = 7 \text{ A}$$

(b) $P_{80i_2} = ?$

$$P_{80i_2} = (5^2)(8)$$

$$P_{80i_2} = 25 \times 8$$

$$P_{80i_2} = 200 \text{ W}$$

$$P_{130i_2} = ?$$

$$P_{130i_2} = (4)^2(13)$$

$$II = 16 \times 13$$

$$II = 208$$

$$P_{40i_1} = ?$$

$$P_{40i_1} = (7)^2(4)$$

$$P_{40i_1} = 49 \times 4$$

$$II = 196 \text{ W}$$

$$P_{40i_2} = ?$$

$$P_{40i_2} = (3)^2(4)$$


$$P_{40i_2} = 9 \times 4$$

$$P_{40i_2} = 36$$

$$P_{200i_1} = (2)^2 R_0 = 4 \times 20$$

$$P_{200i_1} = 80 \text{ W}$$

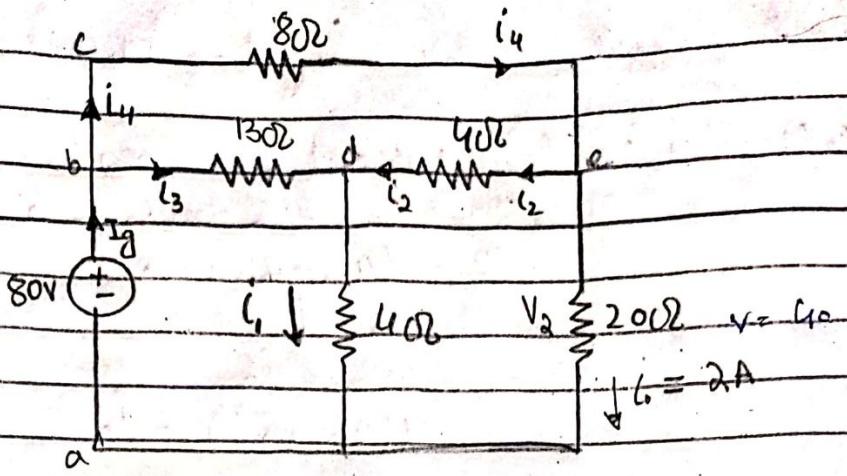Total power absorbed $\approx 200 + 208 + 196 + 36 + 80$
 $\Rightarrow 720 \text{ W}$



(Q)

$$V_2 = (2)(20) = 40 \text{ Volts}$$

Using KVL on left branch,

$$-80 + 13i_3 + 4i_1 = 0$$

$$13i_3 + 4i_1 = 80 \quad (\text{i})$$

Using KVL on another loop

$$-80 + 40 + 4i_2 - 13i_3 = 0$$

$$40 + 4i_2 - 13i_3 = 0$$

$$4i_2 - 13i_3 = -40 \quad (\text{ii})$$

Using KCL at node 'e'

$$-i_2 - 2 + i_4 = 0$$

$$-i_2 + i_4 = 2 \quad (\text{iii})$$

The Voltage drop across 8Ω resistor is
40V

$$\therefore i_4 = \frac{40}{8} = 5 \text{ A put in (iii)}$$

$$-i_2 + 5 = 2$$

$$\therefore i_2 = 2 - 5$$

Using KVL on right branch.

$$i_1(1000) + 4000(i_a) + 3000(i_a) - 2000i_o = 0$$

$$8000i_a - 2000i_o = 0$$

$$2000(4i_a - i_o) = 0$$

$$4i_a - i_o = 0$$

$$4i_a = i_o$$

$$4(2 \times 10^{-3}) = i_o$$

$$i_o = 8 \times 10^{-3} A = 8 \text{ mA} \quad \boxed{\text{(ii)}}$$

(b) $i_g = ?$

Put (ii) in (i)

$$i_g - 8 \times 10^{-3} = 2 \times 10^{-3}$$

$$i_g = 2 \times 10^{-3} + 8 \times 10^{-3}$$

$$\boxed{i_g = 10 \text{ mA}}$$

(c) $P_{\text{dev}} = ?$

Using KVL for V_o

$$-V_o = -(8 \times 10^{-3})(2 \times 10^3) = 0$$


$$-V_o + 16 = 0$$

$$\boxed{V_o = 16 \text{ V}}$$

$$P = -V_o i_g = -16 \times 10 \times 10^{-3} \text{ W}$$

$$\boxed{P = -160 \text{ mW}}$$

PROBLEM 2.21 :-

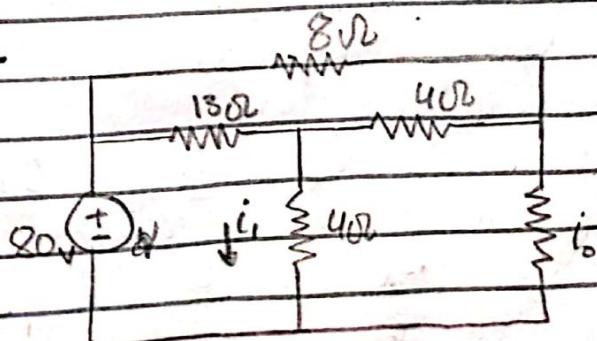

(b) $V_o = ?$

Using KVL on left branch

$$V_o + (80)(2 \cdot 4) = 0$$

$$V_o + 192 = 0$$

$$V_o = -192$$

$$V_o = -\frac{192}{2}$$

$$\boxed{V_o = -192 \text{ V}}$$

(c)

$$P_{diss} = (192)(4) = \boxed{768 \text{ W}}$$

$$P_{80\Omega} = (2 \cdot 4)^2 (80) = 480 \cdot 8 \text{ W}$$


$$P_{30\Omega} = (1 \cdot 6)^2 (30) = 76 \cdot 8 \text{ W}$$

$$P_{90\Omega} = (1 \cdot 6)^2 (90) = 230 \cdot 4 \text{ W}$$

$$\boxed{P_{total} = 768 \text{ W}}$$

PROBLEM 2-202

Sol:-

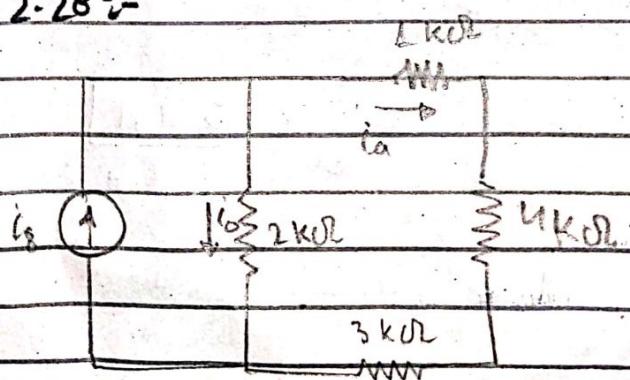

(a)

$$i_g = i_a + i_b$$

$$i_g = (2 \times 10^{-3}) + i_b$$

$$i_g - i_b = 2 \times 10^{-3} \quad (i)$$

$$L_T = L_1 + L_2$$

$$\textcircled{i} \boxed{4A = i_1 + i_2} \quad (\textcircled{i})$$

Using KVL for branch 2

$$30i_2 + 90i_2 - 80i_1 = 0$$

$$120i_2 - 80i_1 = 0$$

$$12i_2 = 8i_1$$

$$i_2 = \frac{8}{12}i_1$$

$$\boxed{i_2 = \frac{2}{3}i_1}$$

Put in \textcircled{i}

$$4 = i_1 + \frac{2}{3}i_1$$

$$4 = \frac{3i_1 + 2i_1}{3}$$

$$\frac{4}{1} = \cancel{\frac{5}{3}}i_1$$

$$5i_1 = 12$$

$$i_1 = \frac{12}{5} = 2.4 \text{ A}$$

Put in \textcircled{i}

$$4 = 2.4 + i_2$$

$$4 - 2.4 = i_2$$

$$\boxed{i_2 = 1.6 \text{ A}}$$

$$5i_a = 2$$

$$i_a = \frac{2}{5} = 0.4 \text{ A}$$

Put in

(b) Put $i_a = 0.4 \text{ A}$ in ①

$$i_b = (0.4)(4) = 1.6 \text{ A}$$

(c) $V_o = ?$

$$V_o = i_b R_{75\Omega}$$

$$V_o = (1.6)(75)$$

$$V_o = 120 \text{ V}$$

(d) $P_{400\Omega} = ?$, $P_{300\Omega} = ?$, $P_{75\Omega} = ?$

$$P_{400\Omega} = i^2 (400)$$

$$P_{300\Omega} = i_a^2 (300)$$

$$P_{75\Omega} = i_b^2 (75)$$

$$P_{400\Omega} = (2)^2 (400)$$

$$P_{300\Omega} = (0.4)^2 (300)$$

$$P_{75\Omega} = (1.6)^2 (75)$$

$$P_{400\Omega} = 160 \text{ W}$$


$$P_{300\Omega} = 48 \text{ W}$$

$$P_{75\Omega} = 192$$

(e) $P_{\text{dev}} = ?$

$$P_{\text{dev}} = (200)(2) = 400 \text{ W}$$

PROBLEM 2.19 :-

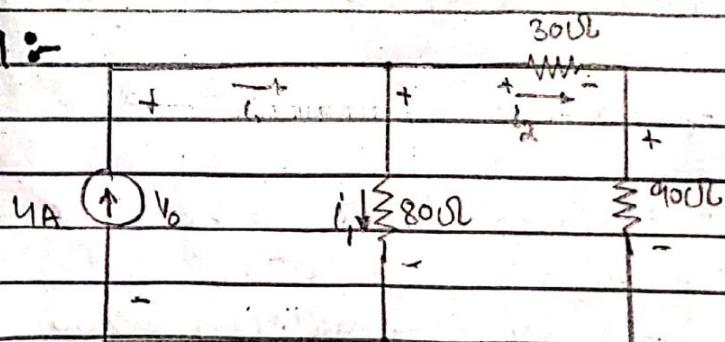

$$i_s = \frac{75}{200} = 375 \times 10^{-3} A = 375 \text{ mA}$$

(e)


The short circuit current is $i_s = 500 \text{ mA}$

(f)

The answer to (d) and (e) is not same b/c of non linearity in the graph.

PROBLEM 2.18:

Sol:

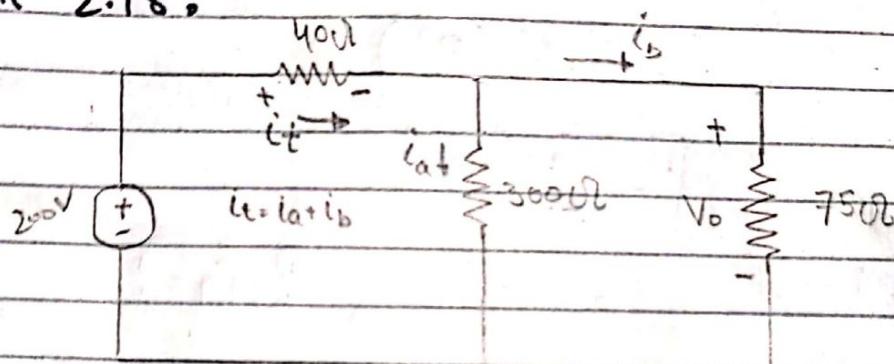

$$V_{300\Omega} = V_{75\Omega}$$

$$\frac{300\Omega \cdot i_a}{75} = \frac{75\Omega i_b}{75}$$

$$i_b = 4i_a \quad (\text{i})$$

Now applying KVL on R-H loops.

$$-200 + i_t(40) + 300i_a = 0$$

$$-200 + (i_a + i_b)40 + 300i_a = 0$$


$$-200 + 40i_a + 40i_b + 300i_a = 0$$

$$-200 + 340i_a + 40i_b = 0$$


$$\Rightarrow 340i_a + 40(i_a) = 200$$

$$340i_a + 160i_a = 200$$

$$\therefore i_a = ? \text{ mA}$$

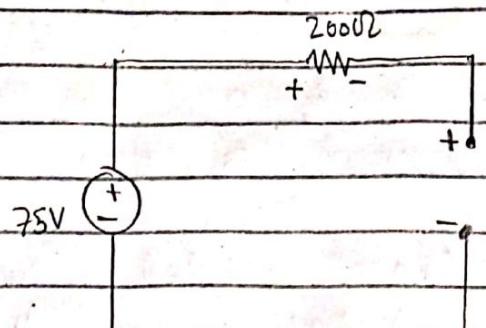

(c)

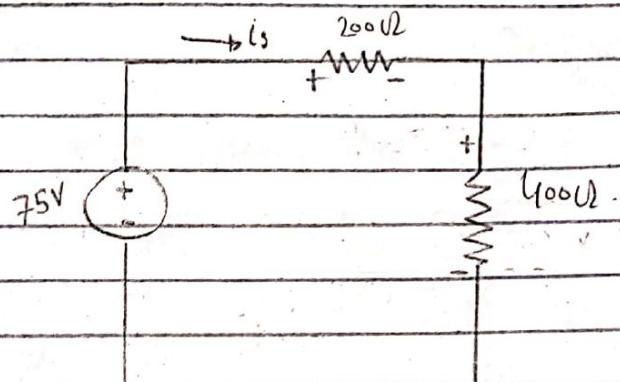

The total voltage drop across 600Ω resistor is equal to the sum of voltage drop across each resistor.


$$\text{i.e } V_s = V_{200\Omega} + V_{400\Omega}$$

$$75 = i_s(200) + i_s(400)$$

$$75 = i_s \cdot 600$$

$$i_s = \frac{75}{600} = 0.125 \text{ A} = 125 \text{ mA}$$

(d)

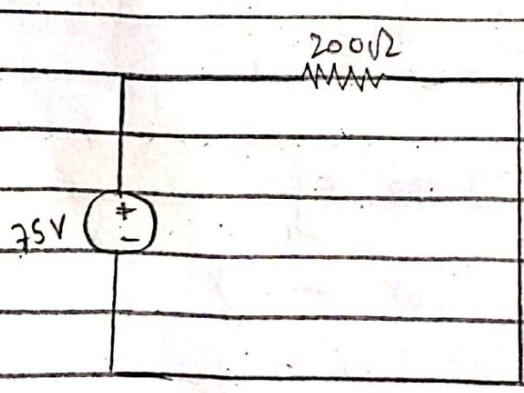

(d)

$$\text{For open circuit, } V_s = (40 \times 10^{-3})(2 \times 10^3) = 80 \text{ V}$$

(e)


When the current $i_s = 0$, the actual open-circuit voltage is 55 V.

(f)

It is b/c linear model cannot predict the non linear behaviour of the practical current source.

PROBLEM 2.17:-

Soli: (a)

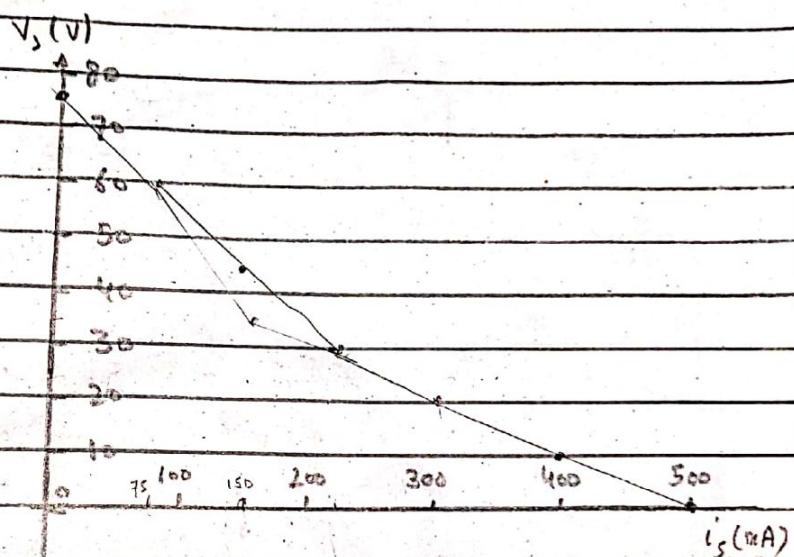

(b)

$$R = \frac{30 - 75}{225 - 0} = \frac{-45}{225 \times 10^3} = -15 \times 10^3 \Omega = -0.2 \text{ m}\Omega$$

$$V_s = -200 \text{ m}\Omega i_s + C \quad (i)$$

When $i_s = 0$, $V_s = 75$ put in (i)

$$75 = -200(0) + C$$

$$C = 75 \text{ V}$$

Put in (i)

$$V_s = -200 \text{ m}\Omega i_s + 75$$

$$V_s + 200 \text{ m}\Omega i_s - 75 = 0$$


(d) For open circuit, $V_s = (4 \times 10^{-3})(2 \times 10^3) = 80$ V

(e) When the current is 0, the actual open-circuit voltage is 55 V.

(f) It is b/c linear model cannot predict the non linear behaviour of the practical current source.

Problem 2.17:-

Sol: (a)

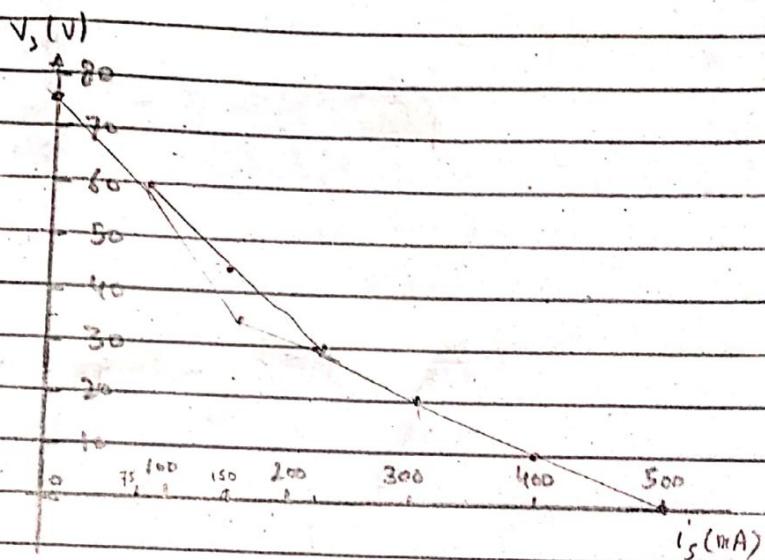

(b)

$$R = \frac{30 - 75}{225 - 0} = \frac{-45}{225 \times 10^3} = -\frac{1}{5 \times 10^3} = -0.2 \Omega \times 10^3 \text{ ohm}$$

$$V_s = -200 \Omega i_s + C \quad (i)$$

When $i_s = 0$, $V_s = 75$ put in (i)

$$75 = -200(0) + C$$


$$\boxed{C = 75 \text{ V}}$$

Put in (i)

$$V_s = -200 \Omega i_s + 75$$

$$V_s + 200 \Omega i_s - 75 = 0$$

(C)

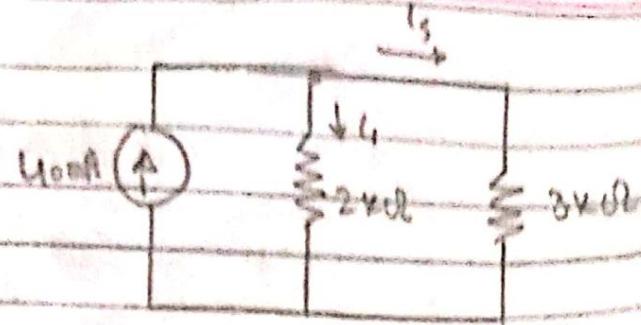

$$10 \times 10^{-3} = i_s + i_1 \quad (\text{Total current in the circuit})$$

Also the potential drop across the terminals of resistor is same.

$$V_S = V_1 \\ (3 \times 10^3) i_S = (2 \times 10^3) i_1$$

$$3i_S = 2i_1$$

$$\left[i_S = \frac{2}{3} i_1 \right] - i_1$$

Put in (i)

$$10 \times 10^{-3} = \frac{2}{3} i_1 + i_1$$

$$10 \times 10^{-3} = \frac{2i_1 + 3i_1}{3} = \frac{5i_1}{3}$$

$$\frac{3}{5} \times 10 \times 10^{-3} = \frac{5}{3} i_1 \times \frac{2}{5}$$

$$i_1 = 24 \times 10^{-3} \text{ A}$$

$$i_1 = 24 \text{ mA}$$


Put in (ii)

$$i_S = \frac{2}{3} (24 \times 10^{-3}) \text{ A}$$

$$i_S = 16 \text{ mA}$$

Ans

Sol:- ① \Rightarrow

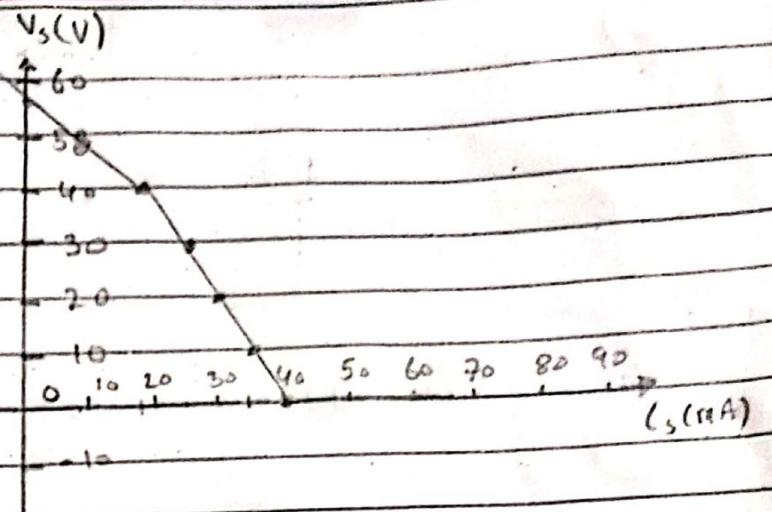

②

$$R = \frac{50}{-40 \times 10^3} = -1375 \times 10^3 \Omega$$

For $0 < V_s \leq 30$ V

$$R = \frac{30 - 0}{(25 - 40) \times 10^3} = \frac{30}{-15 \times 10^3} = -2 \times 10^3 \Omega$$

$$\therefore V_s = -2 \times 10^3 i_s + c \quad \text{--- (i)}$$

$$\text{When } V_s = 0, I_s = 40 \times 10^{-3} \text{ A}$$


$$0 = (-2 \times 10^3)(40 \times 10^{-3}) + c$$

$$0 = -80 + c$$


$$\boxed{c = 80} \quad \text{Put in (i)}$$

$$V_s = -2 \times 10^3 i_s + 80$$

$$V_s + 2 \times 10^3 i_s - 80 = 0$$

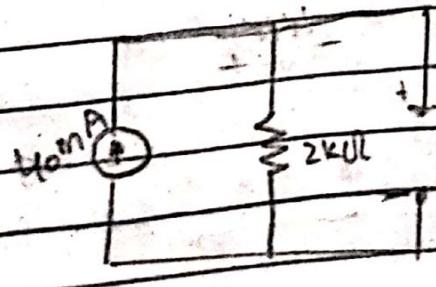

(b)

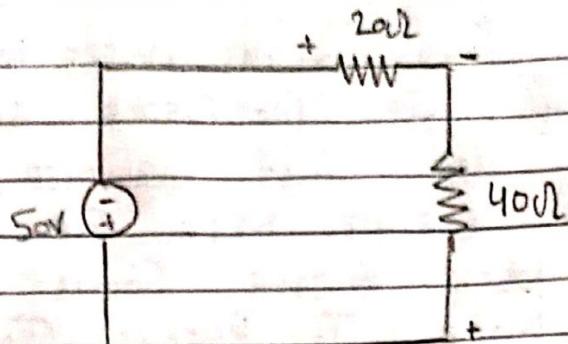

$$50 + 20i_t + 40i_0 = 0 \quad (\text{using kvl})$$

$$50 + 20i_t + 60i_0 = 0$$

$$60i_0 = -50$$

$$i_0 = -\frac{5}{6} = -0.83A$$

$$P_{loss} = R i^2$$

$$P_{loss} = (i_0)(-0.83)^2 = 27.556W$$

P2.16:- THE TABLE BELOW GIVES THE RELATIONSHIP B/W THE TERMINAL CURRENT AND VOLTAGE OF THE PRACTICAL CONSTANT CURRENT SOURCE.

a) PLOT i versus V_s .

b) CONSTRUCT A CIRCUIT MODEL FOR THIS SOURCE THAT IS VALID FOR $0 \leq V_s \leq 30V$ BASED ON THE EQUATION OF THE LINE PLOTTED.

c) USE YOUR CIRCUIT MODEL TO PREDICT THE CURRENT DELIVERED TO A 3Ω RESISTOR?

d) . - - -

e) . - - -


f) . - - -

P2.15: THE VOLTAGE AND CURRENT WERE MEASURED AT THE TERMINALS OF THE DEVICE SHOWN BELOW. THE RESULTS ARE ALSO TABULATED BELOW.

- CONSTRUCT A CIRCUIT MODEL FOR THIS DEVICE USING AN IDEAL VOLTAGE SOURCE AND A RESISTOR.
- USE THE MODEL TO PREDICT THE AMOUNT OF POWER THE DEVICE WILL DELIVER TO A 4Ω RESISTOR.

i_t	V_t (V)	i_t (A)
-30	0	0
10	2	
50	4	
90	6	
130	8	


- Plotting the graph of i_t vs V_t

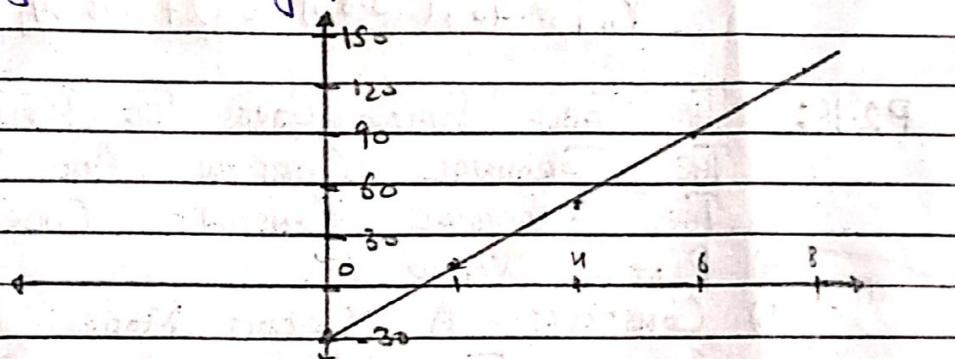

$$R = \frac{160}{8} = 20\Omega$$

When $i_t = 0$, then $V_t = -30$

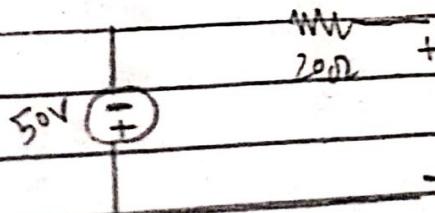$\therefore V = -30$ volts Ideal Voltage Source




$$R = \frac{\text{Total change in } V_t}{\text{Total change in } i_t} = \frac{160}{8} = 20 \Omega$$


When $i_t = 0$, then $V_t = -30$

$$\therefore i = \frac{-30}{20} = -1.5 A$$

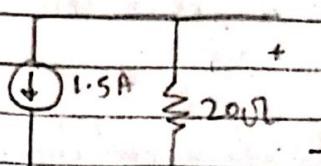\therefore A current source of $1.5 A$ must be connected opposite to the applied voltage V_t .



(b) Attaching a 5Ω resistor

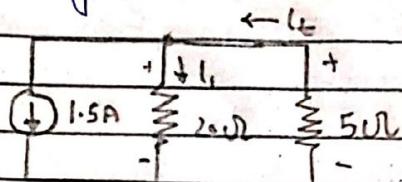

$$-1.5 + i_t = i_1 - i_2 \quad (\text{By using KCL})$$

$$20i_1 - 5i_t = 0 \quad (\text{By using KVL})$$

$$(i) \Rightarrow -1.5 + i_t = i_1$$

$$-1.5 = i_2 - i_t$$

$$i_1 - i_t = -1.5 \quad (\text{iii})$$

$$P_{S1} = (5)(2)^2$$

$$i_t = 2 A$$

$$(ii) = 20i_1 - 5i_t = 0$$

$$5(4i_1 - i_t) = 0$$

$$4i_1 - i_t = 0 \quad (\text{iv})$$

$$2 - i_t = 0$$

$$4(+0.5) - i_t = 0$$

$$\text{Add (iii)} \Rightarrow 4 - 4i_t = -1.5$$


$$\text{(iv)} \Rightarrow +4i_1 - i_t = 0$$

$$\frac{-3i_t = -1.5}{i_t = +0.5 A}$$

Put in N

$$R = \frac{(0.5 \times 10^3)}{1^2} = R = 0.5 \times 10^3 \Omega$$
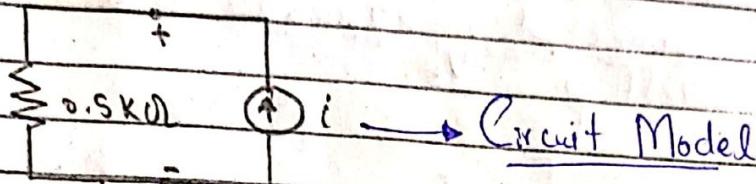
$$R = \frac{2.0 \times 10^3}{(2)^2} = \frac{2.0 \times 10^3}{4} = 0.5 \times 10^3 \Omega$$




P 2-14: THE VOLTAGE AND CURRENT WERE MEASURED AT THE TERMINALS OF THE DEVICE SHOWN BELOW. THE RESULTS ARE TABULATED BELOW.


- CONSTRUCT A CIRCUIT MODEL FOR THIS DEVICE USING AN IDEAL CURRENT SOURCE AND A RESISTOR.
- USE THE MODEL TO PREDICT THE AMOUNT OF POWER THE DEVICE WILL DELIVER TO A 5Ω RESISTOR.

Device	V_t	i	V_t (V)	i (A)
	0	0	-30	0
	10	2	10	2
	50	4	50	4
	90	6	90	6
	130	8	130	8

(a) Plotting graph of i_t vs V_t

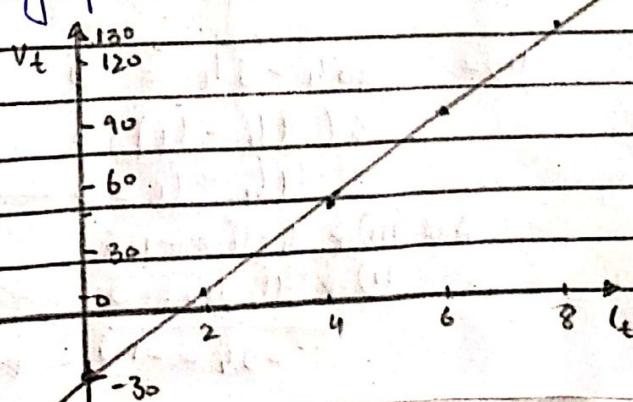


The circuit model is given below

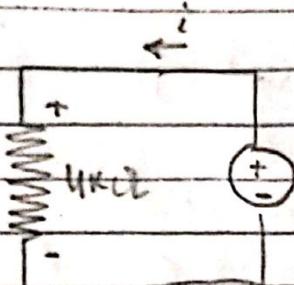

P 2.12:- A VARIETY OF CURRENT SOURCE VALUES WERE APPLIED TO THE DEVICE SHOWN BELOW. THE POWER ABSORBED BY THE DEVICE FOR EACH EACH VALUE OF CURRENT IS RECORDED IN THE TABLE GIVEN BELOW. USE THE VALUES IN THE TABLE TO CONSTRUCT A MODEL FOR THE DEVICE CONSISTING OF A SINGLE RESISTOR.

Sol:-

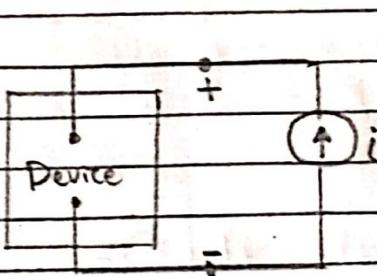

i (A)	P (kW)
1	0.5
2	2.0
3	4.5
4	8.0
5	12.5
6	18.0

We know that


$$P = \frac{V^2}{R} = \frac{(IR)^2}{R} = \frac{I^2 R^2}{R}$$

$$P = I^2 R$$

$$\Rightarrow R = P / I^2$$

Putting values from table.

The circuit model is given below.

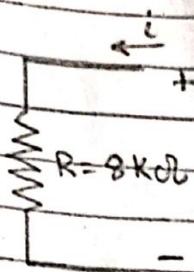

P2.11:- A VARIETY OF Voltage SOURCES WERE APPLIED TO THE DEVICE SHOWN BELOW. THE POWER ABSORBED BY THE DEVICE FOR EACH VALUE OF VOLTAGE IS RECORDED IN THE TABLE GIVEN BELOW. USE THE VALUES IN THE TABLE TO CONSTRUCT A CIRCUIT MODEL FOR THE DEVICE CONSISTING OF A SINGLE RESISTOR.

i	v (V)	p (mw)
	-10	25.0
Device	-5	6.25
	5	6.25
	10	25.0
	15	56.25
	20	100

Sol:-

The equation for resistance in term of Power and Voltage is given by:

$$PR = \frac{V^2}{R} \Rightarrow PR = V^2$$


$$R = \frac{V^2}{P}$$

$$\text{Put } V = -10, P = 25 \times 10^{-3} \text{ W}$$

$$R = \frac{(-10)^2}{25 \times 10^{-3}} = \frac{100}{25 \times 10^{-3}} = 4 \times 10^3 \Omega = 4\text{k}\Omega$$

8

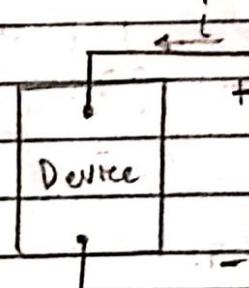P2.10: THE TERMINAL VOLTAGE AND TERMINAL CURRENT WERE MEASURED ON THE DEVICE SHOWN BELOW. THE VALUES OF V AND i ARE GIVEN IN THE TABLE BELOW. USE THE VALUES IN THE TABLE TO CONSTRUCT A CIRCUIT MODEL FOR THE DEVICE CONSISTING OF A SINGLE RESISTOR.



	i (mA)	v (V)
	-20	-160
	-10	-80
Device	10	80
	20	160
	30	240

Ans:-

The Slope is given by:

$$m = R = \frac{(-160) - (-80)}{(-20 \times 10^{-3}) - (-10 \times 10^{-3})}$$


$$R = \frac{-160 + 80}{-20 \times 10^{-3} + 10 \times 10^{-3}}$$

$$R = \frac{-160 - 80}{-10 \times 10^{-3}} = [8 \times 10^3 \Omega]$$

$$\begin{aligned} -V_3 - V_2 + 100 &= 0 \\ -V_3 - V_2 &= -100 \\ V_3 - V_2 &= 100 \quad \text{---(ii)} \end{aligned}$$


Eq(i) and eq(ii) cannot be solved as it includes 3 more unknown voltages.
So the powers cannot be determined and hence energy of this system cannot be determined.

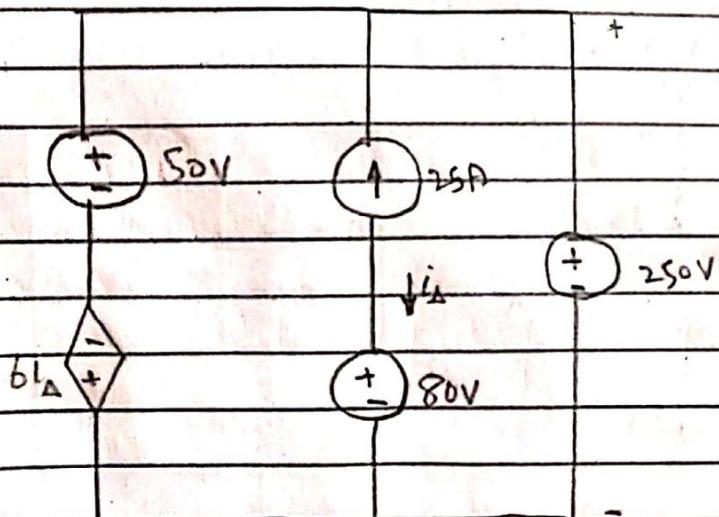P2.8: IF THE INTERCONNECTION IN GIVEN FIGURE IS VALID,
FIND THE TOTAL POWER DEVELOPED IN THE CIRCUIT.
IF THE INTERCONNECTION IS NOT VALID. EXPLAIN WHY?





Sol:- The interconnection is invalid because the voltage drop across each branch is different.

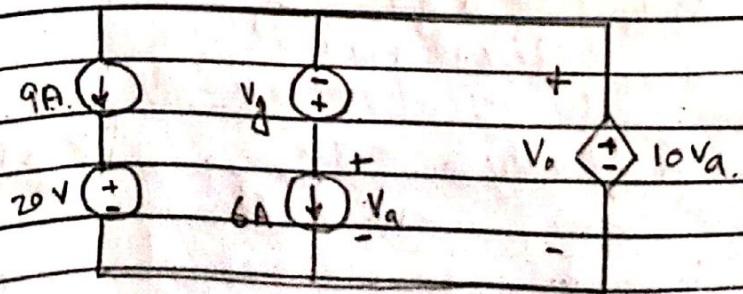P2.9:- FIND THE TOTAL POWER DEVELOPED IN THE CIRCUIT IN GIVEN P FIGURE IF $V_o = 5V$.



Sol:- The interconnection is invalid b/c. the voltage drop on R.H.S is not equal to L.H.S. Moreover, the central junction is also not valid according to KCL. The sum of entering current is not equal to sum of leaving current.

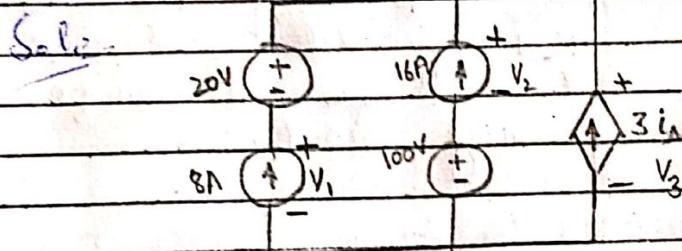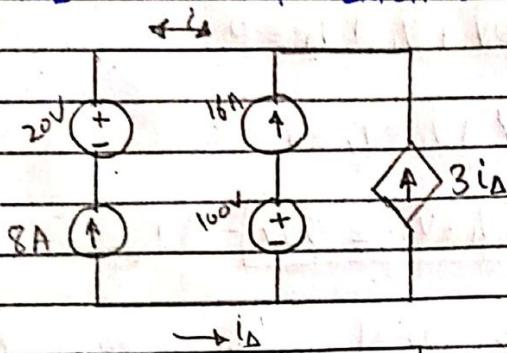P.Q.7:- a) IS THE INTERCONNECTION IN GIVEN FIGURE VALID?
b) CAN YOU FIND THE TOTAL ENERGY DEVELOPED IN THE CIRCUIT? EXPLAIN.




(a) \Rightarrow Yes the interconnection is valid. The current flowing in each loop is same. And the voltage drop at the end points is also same.

(b) \Rightarrow First we will use KVL to find unknown voltage drop, V_1 , V_2 and V_3 .

$$-V_1 - 20 + V_2 + 100 = 0$$

$$-V_1 + V_2 + 80 = 0$$

$$V_1 - V_2 = -80 \quad \text{(i)}$$

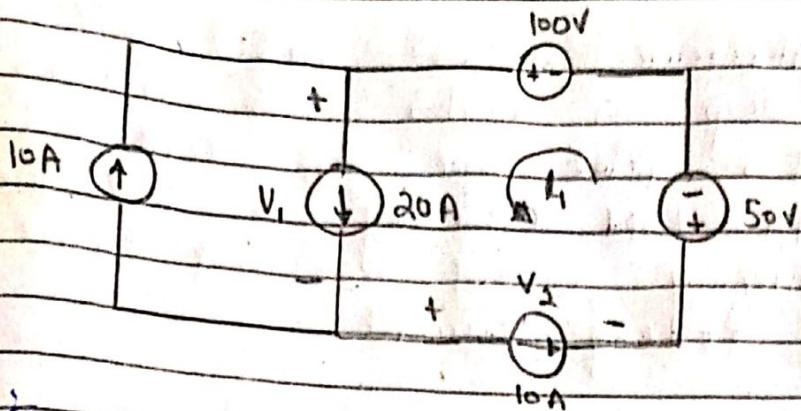

Sol:

= Using KVL for loop II.


$$50V - 100V + V_1 + V_2 = 0$$


$$-50V + V_1 + V_2 = 0$$

$$\boxed{V_1 + V_2 = 50V} \quad \text{---(i)}$$

Equation (i) shows that for any value of V_1 and V_2 , the circuit is valid and their sum is equal to 50V. ∵ It has no unique solution but infinitely many solutions.

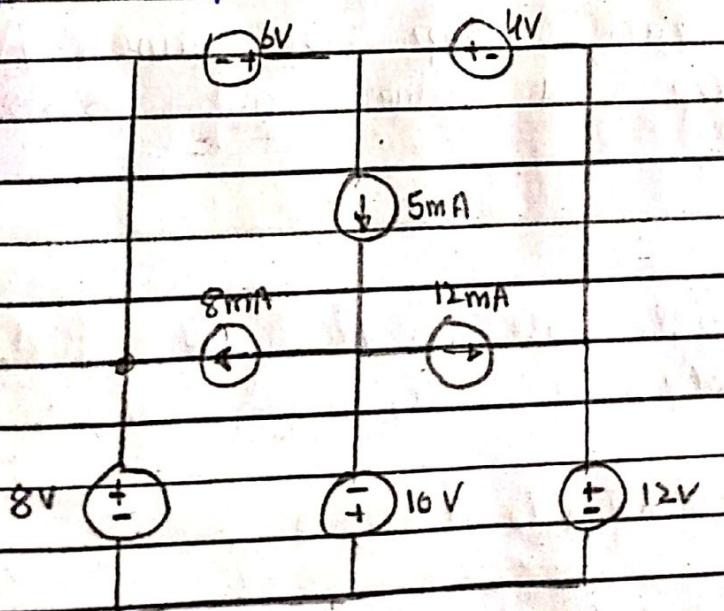P2.6 :- IF THE INTERCONNECTION IN GIVEN FIGURE IS VALID
FIND THE TOTAL POWER DEVELOPED IN THE CIRCUIT.
IF THE INTERCONNECTION IS NOT VALID EXPLAIN WHY?



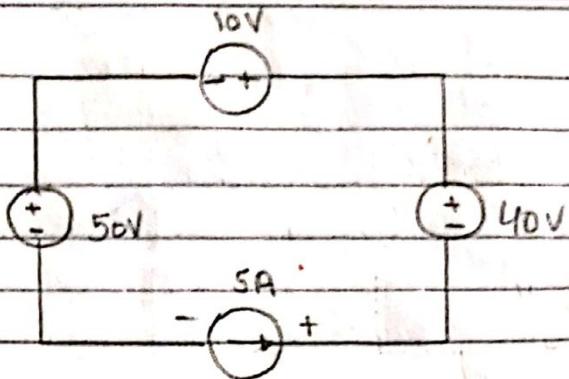

Sol:- First we need to find voltage drop across 5A source.

By using KVL;

$$-40 + 10 + 50 + -V_{5A} = 0$$

$$20 = V_{5A}$$

$$20 = V_{5A}$$

Power associated with each circuit element is.

$$P_{50V} = V_i = (50)(5) \quad P_{10V} = (10)(5) \quad P_{40V} = -(40)(5) \quad P_{5A} = -(2)$$

$$P_{50V} = 250 \text{ W}$$

$$P_{10V} = 50 \text{ W}$$

$$P_{40V} = -200 \text{ W}$$

$$P_{5A} = -10$$

Absorbing


Absorbing

delivering

deliver

Hence, total power absorbed = 300 watt
total power delivered = -300 watt

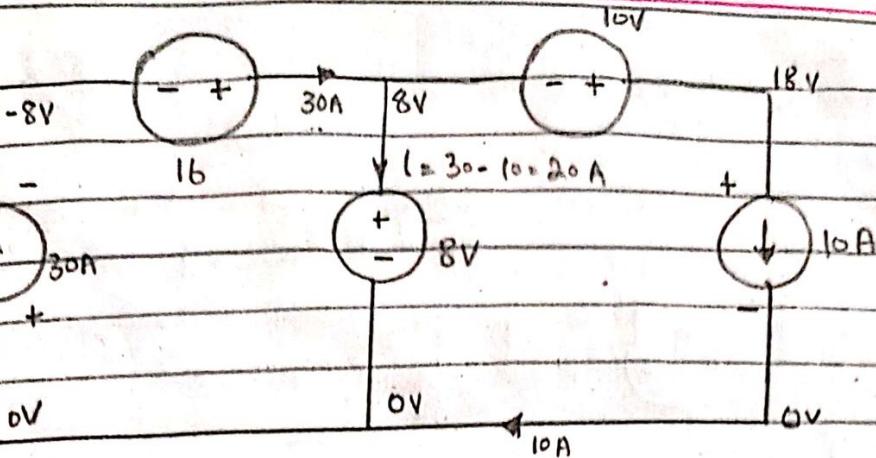
P.s:- THE INTERCONNECTION OF IDEAL SOURCES CAN
TO AN INDETERMINATE SOLUTION. WITH THIS I
IN MIND EXPLAIN WHY THE SOLUTIONS FOR
 V_1 AND V_2 IN THE CIRCUIT IN GENERAL FILE
ARE NOT UNIQUE.



$$P_{30A} = Vi = (30)(8) = 240 \text{ W}$$

$$P_{10A} = Vi = (10)(18) = 180 \text{ W}$$

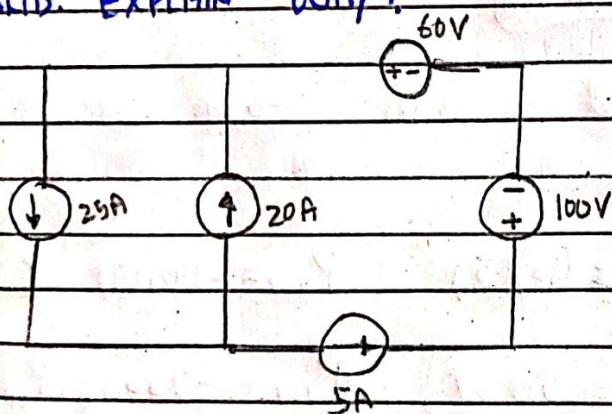Q3.1: IF THE INTERCONNECTION IN GIVEN FIGURE IS VALID
FIND THE TOTAL POWER DEVELOPED BY THE
VOLTAGE SOURCES. IF THE INTERCONNECTION IS NOT
VALID. EXPLAIN WHY?



Ans: The interconnection is invalid, b/c the two current sources supply different amount of current through 100V source.

Q3.4: IF THE INTERCONNECTION IN THE GIVEN FIGURE IS VALID. FIND THE TOTAL POWER DEVELOPED IN THE CIRCUIT. IF THE INTERCONNECTION IS NOT VALID EXPLAIN WHY?

Sols:

P-T-Q

$$P_{18V} = -Vi$$

$$P_{18V} = -(18)(5 \times 10^{-3})$$

$$P_{18V} = -90 \times 10^{-3} W$$

Delivering Power

$$P_{5mA} = +Vi$$

$$P_{5mA} = (5 \times 10^{-3})(5 \times 10^{-3})$$

$$P_{5mA} = 25 \times 10^{-6} W$$

Absorbing Power

$$P_{7V} = +Vi$$

$$P_{7V} = +(7)(5 \times 10^{-3})$$

$$P_{7V} = +35 \times 10^{-3} W$$

Delivering Power
Absorbing Power


\rightarrow Total power absorbed, $\sum P_{abs} = \frac{125 \times 10^{-3} W}{90}$

Total power delivered, $\sum P_{del} = (-90 \times 10^{-3})$

$H \cdot H \cdot H \cdot H = -125 \times 10^{-3} W$

As $eq(1) + eq(2) = 0 \Rightarrow$ The power delivered is equal to power absorbed.

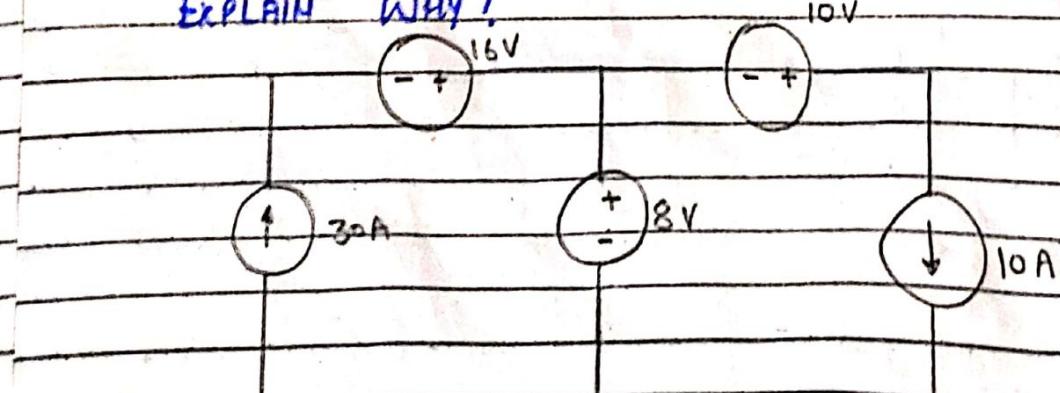
P2.2: IF THE INTERCONNECTION IN BELOW FIGURE IS VALID,
FIND THE POWER P DEVELOPED BY THE CURRENT SOURCES. IF THE INTERCONNECTION IS NOT VALID.
EXPLAIN WHY?



Sol: The circuit connection is valid.

The detailed diagram is given on next page.

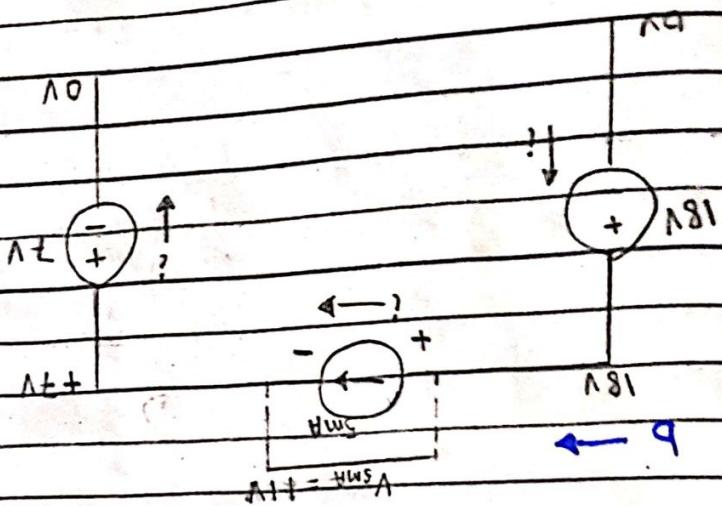The expression for power associated with each element is given by



Q) Yes, the circuit is valid.

As eq(i) + eq(ii) = 0 ∴ The power delivered is equal to power absorbed.

$$\text{Total Power delivered, } \Sigma P_{\text{del}} = [-185 \times 10^{-3} \text{ Watts}]$$

$$\text{Total Power absorbed, } \Sigma P_{\text{abs}} = [125 \times 10^{-3} \text{ Watts}]$$

∴ Total Power absorbed, $\Sigma P_{\text{abs}} = (90 \times 10^{-3}) + (35 \times 10^{-3})$

Absorbing Power	Delivering Power	Absorbing Power	Delivering Power
$P_{\text{abs}} = 90 \times 10^{-3} \text{ Watts}$	$P_{\text{del}} = 125 \times 10^{-3} \text{ Watts}$	$P_{\text{abs}} = 35 \times 10^{-3} \text{ Watts}$	$P_{\text{del}} = -185 \times 10^{-3} \text{ Watts}$
$P_{\text{abs}} = (5 \times 10^{-3})(18)$	$P_{\text{del}} = (5 \times 10^{-3})(25)$	$P_{\text{abs}} = (3 \times 10^{-3})(5)$	$P_{\text{del}} = -125 \times 10^{-3} \text{ Watts}$
$P_{\text{abs}} = iV$	$P_{\text{del}} = -iV$	$P_{\text{abs}} = iV$	$P_{\text{del}} = iV$

The expressions for power delivered with each element is given as follows

CHAPTER 2 - PROBLEMS


Section 2.1 :-

P 2.1 :- a) IS THE INTERCONNECTION OF IDEAL SOURCES IN THE CIRCUIT IN FIG VALID? EXPLAIN.


b) IDENTIFY WHICH SOURCES ARE DEVELOPING POWER AND WHICH SOURCES ARE ABSORBING POWER.

c) VERIFY THAT THE TOTAL POWER DEVELOPED IN CIRCUIT EQUALS THE TOTAL POWER ABSORBED.

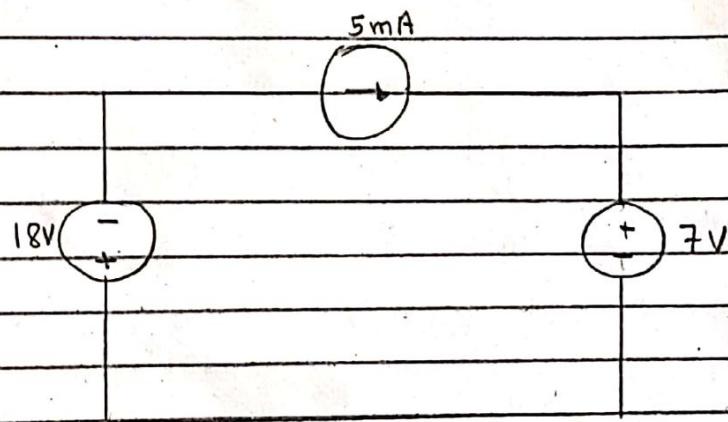d) REPEAT (a)-(c). REVERSING THE POLARITY OF THE 18V SOURCE



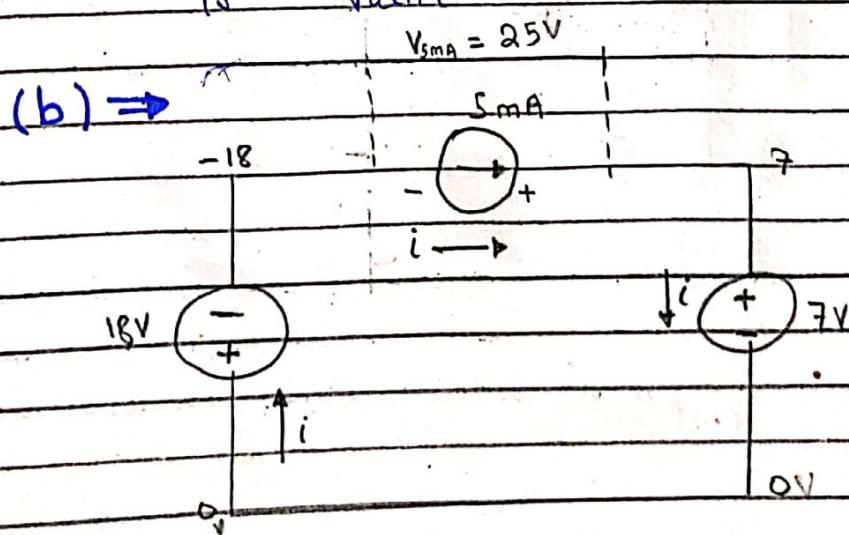Sol:- (a) \Rightarrow Yes, by definition of independent voltage sources, the interconnection is valid.



$$(b) i_g = i_A + i_S + 8i_D = 9i_A + i_S = 47 \text{ A}$$

$$V_d = 80 - 20 = 60 \text{ V}$$

$$\sum P_{\text{diss}} = -4230 \text{ W}$$

$$\sum P_{\text{gen}} = 4230 \text{ W}$$

P 2.32 :-

$$\text{Sol: } i_B = \frac{(V_{cc} R_2) / (R_1 + R_2) - V_o}{(R_1 R_2) / (R_1 + R_2) + (1 + \beta) R_E}$$

$$\frac{V_{cc} R_2}{R_1 + R_2} = \frac{(15)(80)}{100} = 12$$

$$\frac{R_1 R_2}{R_1 + R_2} = \frac{20 \times 80}{100} = 16000 \Omega = 16 \text{ k}\Omega$$

$$i_B = \frac{12 - 0.2}{16 + 40(6.1)} = \frac{11.8}{20} = 0.59 \text{ mA}$$

$$i_C = \beta i_B = 39 \times 0.59 = 23.01 \text{ mA}$$

$$i_E = i_C + i_B = 23 + 0.59 = 23.59 \text{ mA}$$

$$V_{sd} = (23.6)(0.1) = 2.36 \text{ V}$$

$$V_{bd} = V_o + V_{sd} = 2.56 \text{ V}$$

$$i_2 = \frac{V_{bd}}{R_2} = \frac{2.56 \times 10^{-3}}{80} = 32 \mu\text{A}$$

$$i_A = i_2 + i_B = 32 + 59 = 622 \mu\text{A}$$



$$V_{ab} = 20(6,622) \approx 12.0 \mu\text{V}$$

$$i_{cc} = i_c + i_1 = 23.01 + 0.622 = 23.632 \text{ mA}$$

$$V_{13} + 23.01(0.5) + 2.36 = 15$$

$$V_{13} = 1.135 \text{ V}$$

PROBLEM 2.33 :-

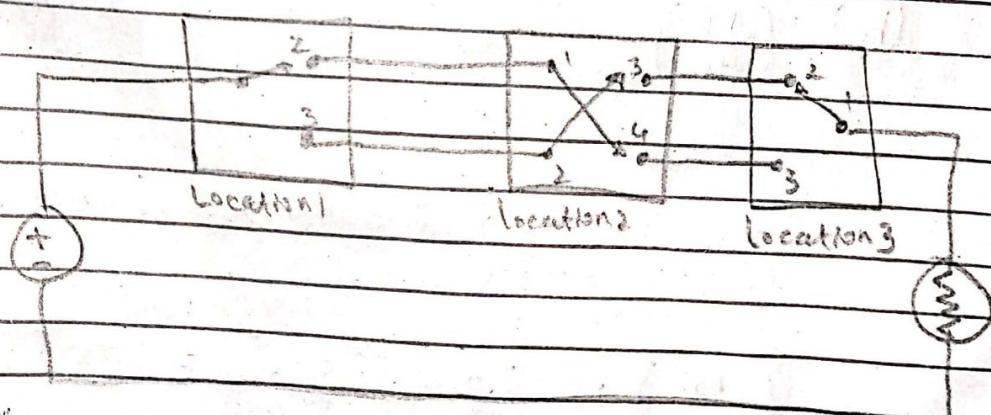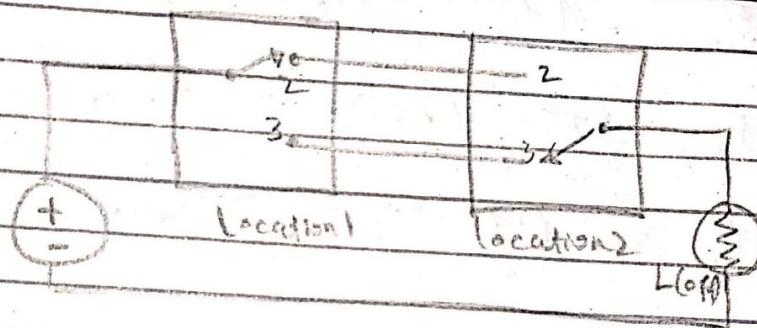

P 2.34 :-


Sol: Using Ohm's Law and KVL.

$$400i + 50i + 200i - 256 = 0$$

$$\text{hence } i = \frac{250}{650} = 385 \text{ mA}$$

This current is nearly enough to stop the heart so a warning sign should be posted at the 250V source.

P 2.35 :-

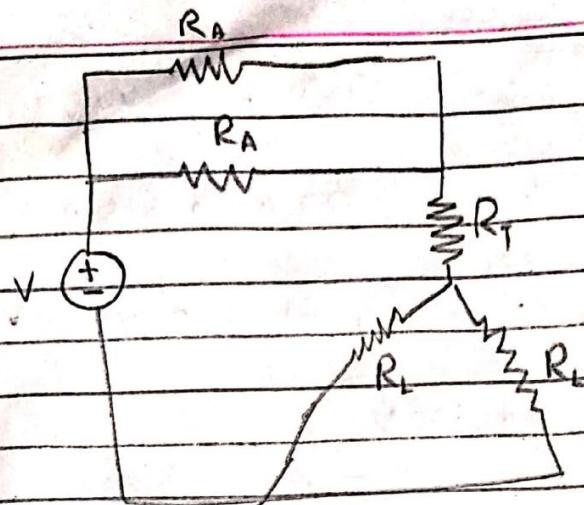

P 2.36 :-

$$(a) P_{arm} = \left(\frac{250}{650}\right)^2 (400) = 54.19 \text{ W}$$

$$P_{leg} = \left(\frac{250}{650}\right)^2 (200) = 29.59 \text{ W}$$

$$P_{trunk} = \left(\frac{250}{650}\right)^2 (50) = 7.4 \text{ W}$$

$$(b) \left(\frac{dT}{dt}\right)_{arm} = \frac{2.39 \times 10^{-4} P_{arm}}{4} = 35.36 \times 10^{-4} \text{ }^{\circ}\text{C/s}$$

$$t_{arm} = \frac{5}{35.36} \times 10^4 = 1414.23 \text{ s or } 23.57 \text{ min}$$

$$\left(\frac{dT}{dt}\right)_{leg} = \frac{2.39 \times 10^{-4}}{10} P_{leg} = 7.07 \times 10^{-4} \text{ }^{\circ}\text{C/s}$$

$$t_{leg} = \frac{5 \times 10^4}{7.07} = 7,071.13 \text{ s or } 117.85 \text{ min}$$

$$\left(\frac{dT}{dt}\right)_{trunk} = \frac{2.39 \times 10^{-4} (7.4)}{25} = 0.71 \times 10^{-4} \text{ }^{\circ}\text{C/s}$$

$$t_{trunk} = \frac{5 \times 10^4}{0.71} = 70,422.54 \text{ s or } 1,173.71 \text{ min}$$

(c) They are all much greater than a few minutes.

P 2.37 :- (a) $R_{\text{arms}} = 400 + 400 = 800 \Omega$

$$i_{\text{safe}} = 50 \text{ mA (min)}$$

$$V_{\text{min}} = 800 \times 50 \times 10^{-3} = 40 \text{ V}$$

(b) No, $12/800 = 15 \text{ mA}$. This current is sufficient to give a perceptible shock.

P 2.38 :-

$$R_{\text{space}} = 1 \text{ M}\Omega$$

$$i_{\text{space}} = 3 \text{ mA}$$

$$\text{Q}_0 \quad V = i_{\text{space}} R_{\text{space}}$$

$$V = 3000 \text{ V}$$