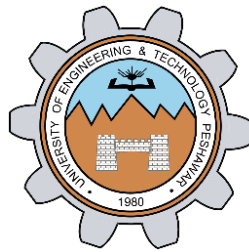


## **Circuit and System-I**

### **LAB # 04**



**Spring 2022**

Submitted by: Ali Asghar

Registration No.: **21PWCSE2059**

Class Section: **C**

“On my honor, as student of University of Engineering and Technology, I have neither given nor received unauthorized assistance on this academic work.”

Student Signature: \_\_\_\_\_

Submitted to:

**Engr. Faiz Ullah**

19 May, 2022

Department of Computer Systems Engineering

## ASSESSMENT RUBRICS LAB # 04

### Verification of Ohm's law Using Bread-Board

LAB REPORT ASSESSMENT				
Criteria	Excellent	Average	Nil	Marks Obtained
<b>1. Objectives of Lab</b>	All objectives of lab are properly covered [Marks 1]	Objectives of lab are partially covered [Marks 0.5]	Objectives of lab are not shown [Marks 0]	
<b>2. Ohm's Law and Mathematical Expression.</b>	Correct definition of Ohm's law, mathematical expression and circuit diagram is shown. [Marks 1]	Correct statement of Ohm's law and no mathematical expression and circuit diagram with no labels. [Marks 0.5]	No definition, mathematical expression and circuit diagram is shown [Marks 0]	
<b>3. Apparatus Used</b>	All equipment and electrical components used are shown [Marks 1]	Equipment and electrical components are partially shown and some of the components are missing [Marks 0.5]	Equipment and electrical components used are not shown [Marks 0]	
<b>4. Procedure</b>	All experimental steps are shown in detail [Marks 2]	Some of the experimental steps are missing [Marks 1]	Experimental steps are missing [Marks 0]	
<b>5. Observations &amp; Calculations</b>	All experimental results are completely shown in form of table and error calculation between theoretical and practical values are also shown. [Marks 2]	Experimental results are partially shown and some of the observations are missing. [Marks 1]	No experimental results are shown [Marks 0]	
<b>6. Graphs</b>	Graphs from experimental results of Ohm's law using theoretical and practical are shown with labels. [Marks 2]	Graphs from experimental results of Ohm's law are shown with no labels and no comparison of theoretical and practical values. [Marks 1]	No graphs are shown [Marks 0]	
<b>7. Conclusion</b>	Conclusion about experimental results is properly explained and satisfactory. [Marks 1]	Conclusion about experimental results is not properly explained and satisfactory. [Marks 0.5]	No conclusion is shown [Marks 0]	

Total Marks Obtained: \_\_\_\_\_

Instructor Signature: \_\_\_\_\_

**TITLE:**

Verification of **OHM'S LAW** using **BREADBOARD**

**OBJECTIVES :**

- ❖ To verify ohm's law through practical experiment.

**APPARATUS:**

- 1) Power supply
- 2) Breadboard
- 3) Wires
- 4) Digital Multimeter
- 5) Resistor

**OHMS LAW:**


**DEFINITION:**

Ohm's law states that the current in an electric circuit is proportional to the applied voltage and inversely proportional to its resistance.

**MATHEMATICAL EXPRESSION:**

$$V = IR$$

**CIRCUIT DIAGRAM :**

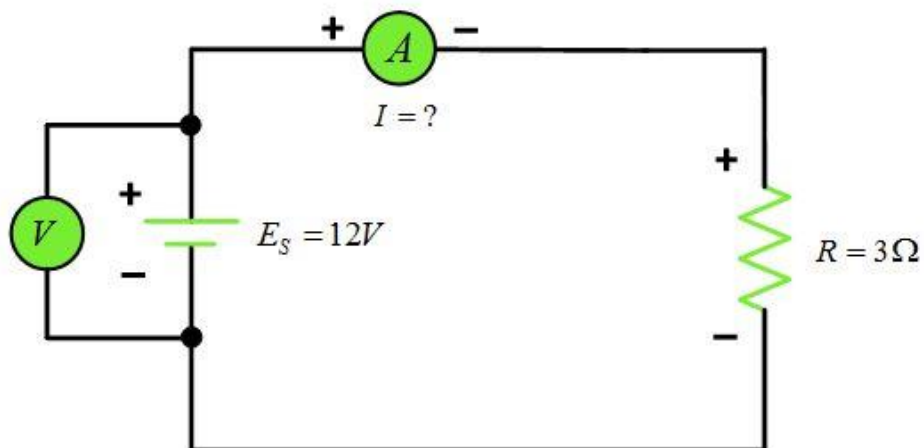


**PROCEDURE:**

- 1) First we connect the components and the wires according to the circuit diagram as given below:
- 2) We set the power supply at certain voltage and then measure the current through digital multimeter.
- 3) Repeat the previous step several times and then graph all the values.
- 4) If the graph is straight line then this verifies the ohm's.

**OBSERVATION:**

S.No.	Voltage(V)	Current(I)
1	5	312.5 $\mu$ A
2	10	625.00 $\mu$ A
3	15	937.50 $\mu$ A
4	20	1.250 mA
5	25	1.563 mA
6	30	1.875 mA

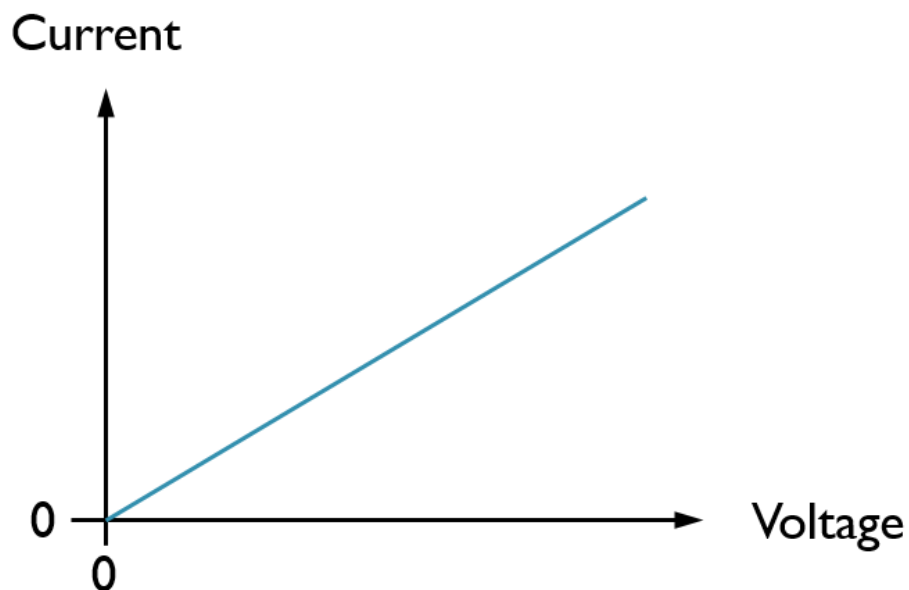**GRAPH:****THEORITICAL GRAPH:**

## **PRACTICAL GRAPH:**

