

Experiment No. 01:-

To find Resistance of Galvanometer by Kelvin's Method.

Galvanometer:-

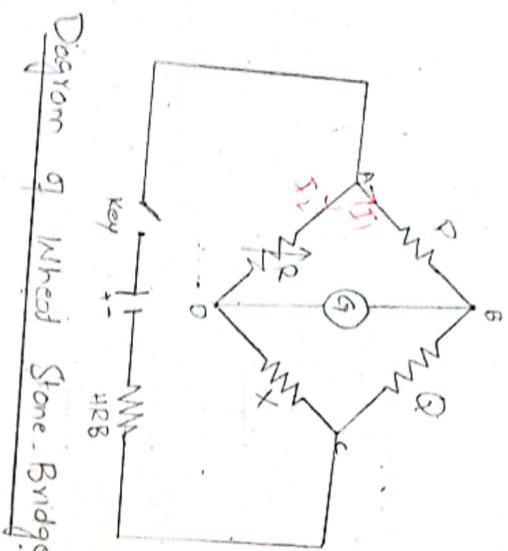


Diagram of Wheat Stone Bridge.

The above equation shows that current in galvanometer is directly proportional to angle of deflection of scale.

Wheat Stone Bridge:

It is the device used to calculate and find unknown resistance is called Wheat Stone Bridge.

Mathematically:-

$$X = \frac{RQ}{P}$$



where 'X' is unknown resistance.

Post Office Box:

It is a device which works on the same principle of Wheat Stone Bridge

Principle of Experiment:-

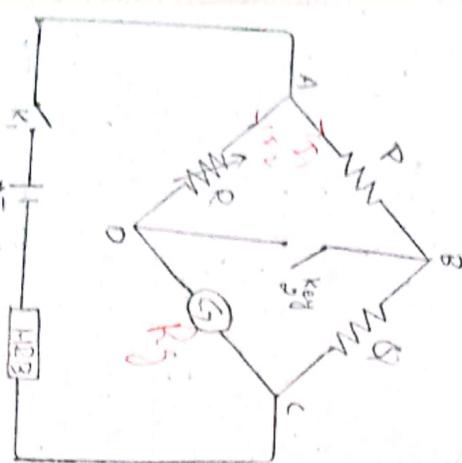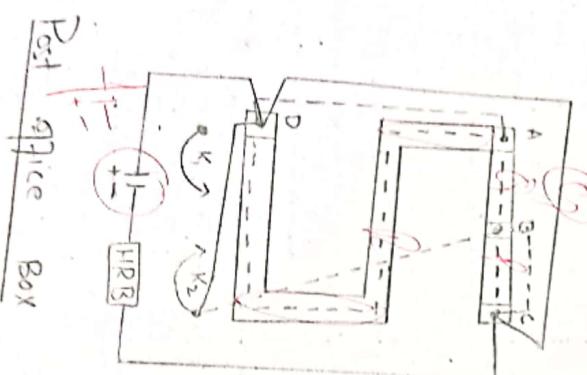Dotted lines are hidden connections and straight line are connection q



Observations and Calculations

S.No	P (Ω)	Q (Ω)	R (Ω)	$R_g = \frac{QR}{P}$
1	100 Ω	10 Ω	1000 Ω	$\frac{(10)(1000)}{100} = 100 \Omega$
2	1000 Ω	100 Ω	1100 Ω	$\frac{(1000)(100)}{1000} = 100 \Omega$
3	10 Ω	10 Ω	100 Ω	$\frac{(10)(100)}{10} = 100 \Omega$
4	1000 Ω	1000 Ω	100 Ω	$\frac{(1000)(100)}{1000} = 100 \Omega$
5	100 Ω	100 Ω	100 Ω	$\frac{(100)(100)}{100} = 100 \Omega$
6	110 Ω	100 Ω	110 Ω	$\frac{(110)(100)}{110} = 100 \Omega$

Q? P?

where we will use the following formula
 $X = R_g = \frac{RQ}{P}$

Apparatus :-

- ↳ Galvanometer
- ↳ Connecting Wires
- ↳ High Resistance Box
- ↳ Battery
- ↳ Post Office Box

Procedure of Experiment :-

- 1) First insert P and Q resistance.
 - 2) Connect K, and note the deflection. If it shows no deflection check for loose wires, key etc.
 - 3) Insert resistance from H.R.B for with in scale deflection e.g. $\theta = 20^\circ$.
 - 4) Now connect K. If the scale show no deflection circuit is balanced. Now note the reading of P, Q and R to find R_g . If circuit shows deflection then balance it by applying more resistance from R.
 - 5) Find R_g by using mathematical expression
- $$R_g = \frac{RQ}{P}$$

Pre class

B

Experiment No. 02.

Conversion of Galvanometer into Ammeter
(Range 0-40 mA, 0-50 mA, 0-60 mA)

Ammeter:-

An ammeter is a measuring device used for the measurement of current in a circuit. It has a very small internal resistance.

Shunt Resistance :-

Shunt resistance is usually small resistance ranging from 1 to 100 or 500 ohms. It is represented by R_s .

Fractional Resistance:-

Fractional resistance is very small resistance and is in fractions like $0.1, 0.2$ ohms etc.


Principle of Experiment:-

The principle of experiment is when a shunt resistance is connected with galvanometer in parallel it is converted to Ammeter.

Apparatus:-

- ↳ Galvanometer
- ↳ Ammeter
- ↳ Voltmeter
- ↳ High Resistance Box

Figure 01

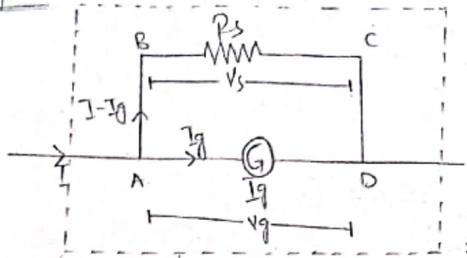

Conversion of Galvanometer into Ammeter

For Circuit

↳ Small Resistance Box
↳ Fractional Resistance Box

↳ Connecting Wires
↳ Battery



$$(I - I_g)R_s = I_g R_g$$

$$R_s = \frac{I_g R_g}{I - I_g}$$

where R_s is Shunt resistance of circuit

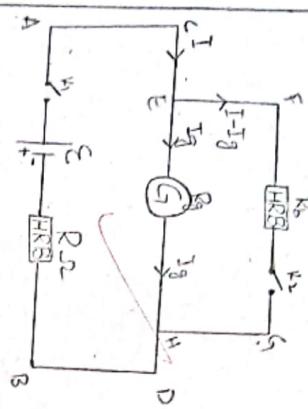


Table for value of R_g (R_g)

S.No	R_s	I_g	$R_g = \frac{I_g}{I_s}$	$R_g (m\Omega)$	$R_g = \frac{I_g}{I - I_g} (m\Omega)$
1	7000 m Ω	10	9.5	120 m Ω	$R_g = 120 m\Omega$
2	8000 m Ω	17	8.5	140 m Ω	$R_g = 140 m\Omega$
3	10,000 m Ω	14	7	140 m Ω	$R_g = 140 m\Omega$
4	5000 m Ω	30	15	140 m Ω	$R_g = 140 m\Omega$
5	10,700 m Ω	13	6.5	130 m Ω	$R_g = 130 m\Omega$

For one value we will take Average value
 $\langle R_g \rangle = 134 m\Omega$

R_g By Half Deflection Method

Procedure of Experiment:

The experiment is performed in

the following steps.

Step: 1: Calculating Resistance of galvanometer by half deflection method.

i) Connect the circuit as shown in figure. or

ii) First insert key 1 and note initial Deflection of galvanometer. It should be out of scale.

iii) Apply resistance from R box with in scale deflection.

iv) Note the current deflection of galvanometer as θ_1 .

v) Now plug key 2. The deflection of galvanometer should be zero.

vi) Apply resistance from R box till the deflection of galvanometer become equal to half of θ_1 i.e $\theta_2 = \theta_1/2$

vii) Note the resistance in R box which is equal to resistance of galvanometer R_g .

Step No. 2: Calculating current through galvanometer (I_g) by full deflection method.

i) Connect the circuits as shown in figure 03.


ii) Find the emf of the battery connected to circuit

For Shunt Resistance

$$R_s = \frac{I_g R_g}{I - I_g}$$

$$R_s = \frac{(0.3 \times 10^{-3} \text{ A})(134 \text{ A})}{(30 \times 10^{-3} \text{ A} - 0.3 \times 10^{-3} \text{ A})}$$
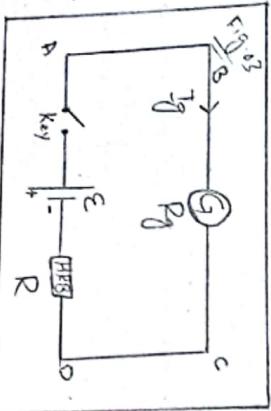
$$R_s = \frac{40 \times 10 \times 10^3 \text{ A}}{29.7 \times 10^3 \text{ A}}$$



value of I_g by Full Deflection Method

Table For value of I_g .

S.No	R_g	R	E	$I_g = \frac{E}{R+R_g}$
1	134 mico	1kW	1.1V	$\frac{1.1}{134 + 1000} = 0.3 \text{ mA}$

So the value of $I_g = 0.3 \text{ mA}$ or $30.8 \times 10^{-6} \text{ A}$

Here I was the range/maximum current measured by ammeter.

- v- Apply resistance from HRB for with in scale terminals to it.
- v- Insert key and note the deflection of galvanometer. The deflection should be out of scale.

v- Apply resistance from HRB for with in scale terminals to it.

- v- R_g is already calculated in above step so find the current in galvanometer by using formula $I_g = \frac{E}{R+R_g}$.

Step No. 0.3:- Calculation of Shunt Resistance.

- v- Shunt resistance is calculated through a formula $R_s = I_g R_g / (I - I_g)$.

v- Now connect the circuit as shown in figure number 04.

- v- Insert key and note the deflection of the galvanometer after applying R_s resistance.


v- You must select range for your galvanometer for comparison with ammeter for verification of result.

- v- Note the current in Ammeter connected (I_s)

v- Now also note the deflections in galvanometer and count divisions (dr)

- v- Find I_c by using formula $I_c = \frac{R_s}{R+R_s} I_s$

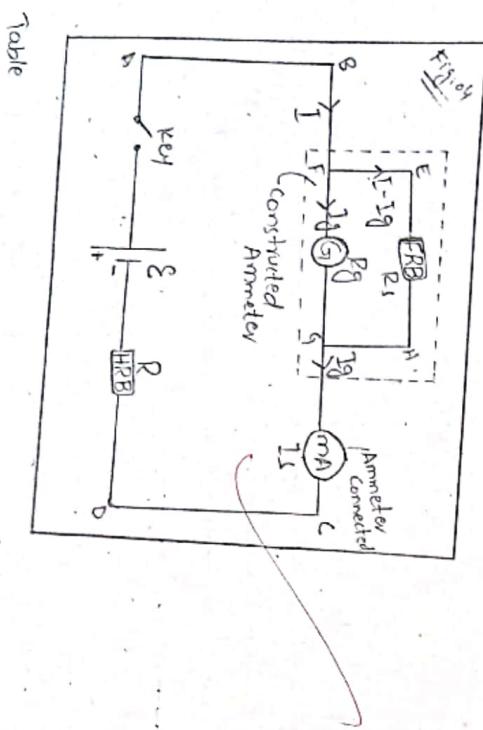v- For galvanometer that has maximum 30 digits



Table

S.No	R_g	I_s (mA)	δ (div)	$I_c = \frac{R_s}{R+R_s} I_s$	Error $\frac{\delta - I_c}{I_c} \times 100\%$
1	5000	19mA	26div	$I_c = \frac{20}{30} \times 26 = 26 \text{ mA}$	7.6m%

Result:- Hence we constructed an Ammeter of Range (0-30 mA)

iii- Now find the error in both circuits by using formula $I_c - I_s$.

Precautions for Experiment:

- i- Use one new battery or power source.
- ii- Source should be fully charged.
- iii- Take Galvanometer and Ammeter without zero error.
- iv- Try to keep length of shunt resistance same in parallel with galvanometer.
- v- Connect the wires and keys tight to minimize error probability in reading.
- vi- Do not alter or change galvanometer or Ammeter while experimenting.

A +

A -

Experiment No: 03:-

Conversion of Galvanometer in Voltmeter

a) Range 3-4 volts.

Voltmeter:-

It is an instrument used for the measurement of electric potential or potential difference between two points. It is connected across the component's ends, potential difference across which is to be measured.

Principle of Experiment:-

When a high resistance is connected with a galvanometer in series, then the galvanometer acts as voltmeter.


Mathematically:-

$$V = V_g + V_H$$
$$V = I_g R_g + I_g R_H \Rightarrow I_g (R_g + R_H)$$

$$\frac{V}{I_g} = R_g + R_H$$

$R_H = \frac{V}{I_g} - R_g$ where "V" is range of constructed voltmeter.


Figure of

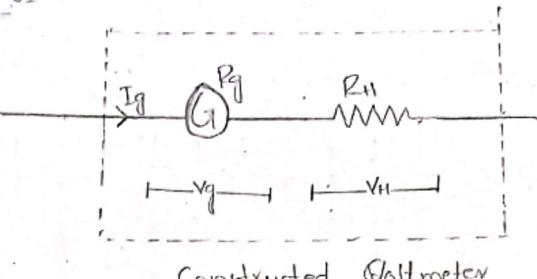

Constructed Voltmeter

Apparatus:-

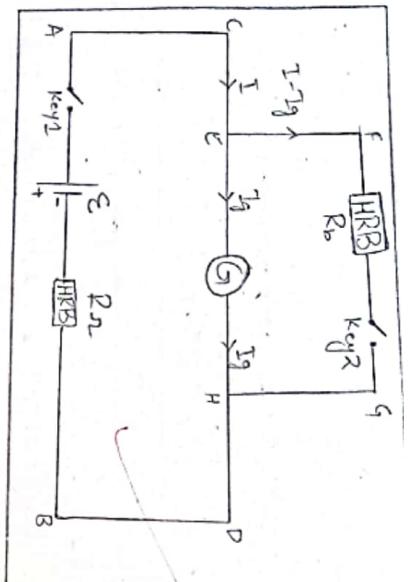- ↳ Galvanometer
- ↳ HRB Boxes
- ↳ Voltmeter
- ↳ Connecting Wires
- ↳ Battery
- ↳ Keys
- ↳ Shunt Resistance Box



Rg By Half-Deflection Method


Table For Value of Rg

S.No	R _b	$\frac{Q_1}{2}$	$\frac{Q_1}{2}$ (A)	R _b = R _g (Ω)
1	7000 Ω	17	8.5	120 Ω
2	10,000 Ω	12	6	110 Ω
3	5000 Ω	24	12	120 Ω

So To find R_g we will Take Average

$$\langle R_g \rangle = 116.6 \Omega$$

Figure 03

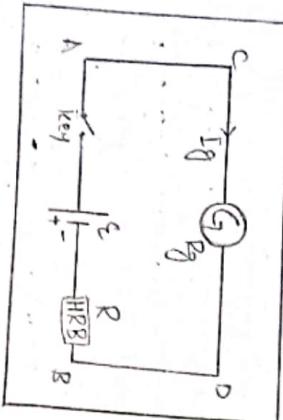

Ig By Full-Deflection Method

Procedure of Experiment:-

The total procedure of experiment

consist of following steps.

Step No.01:- Calculating Resistance of galvanometer by half-Deflection Method.

i- Connect the circuit according to figure 02

ii- Insert key 1 and note deflection of galvanometer. It should be out of scale.

iii- Apply resistance from R_b with in scale deflection.

iv- Note the current deflection of galvanometer as Q₁.

v- Note plug key 2. Note deflection of galvanometer. It should be zero.

vi- Apply resistance from galvanometer from R_b till the current deflection Q₂ became equal to half of Q₁ i.e. Q₂ = Q₁/2

vii- Note the resistance of R_b which is equal to the resistance of galvanometer R_g.

Step No.02:- Calculating current through galvanometer (Ig) by full deflection Method.

i- Connect the circuit according to figure 03.

ii- Find the emf of connected battery with the help of voltmeter by connected the both terminals to it.

iii- Insert key and note deflection of galvanometer. It should be out of scale.

Table For value of $\frac{V_g}{I_g}$:

S.No	R_g	R	E	$I_g = \frac{E}{R+R_g}$
1	116.6	3900	1.3V	0.3mA

Now we have

$$R_H = \frac{V}{I_g} - R_g \Rightarrow \frac{3}{0.3 \times 10^{-3}} \times 116.6 \Omega$$

$$R_H = 10,000 - 116.6 \Rightarrow [9883.4 \Omega]$$

Figure 04

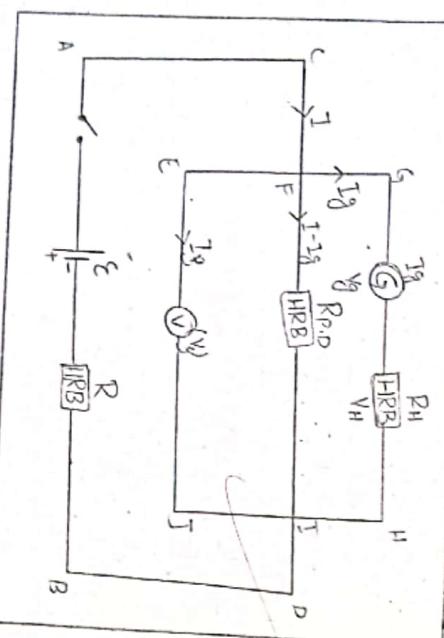


Table For V_g :

S.No	$V_g(v)$	Div_g	$V_g = \frac{R_H \times \text{Div}_g}{30}$	Error
1	0.75V	7.5div	$\frac{3}{30} \times 7.5 = 0.75(V)$	0

Result:- Hence we constructed a voltmeter
of Range 0-3 volts.

Precautions of Experiments:-
1. The power source or battery should be fully charged.

v- Apply resistance from HPB for ~~High~~ in scale deflection till the needle reach to maximum deflection of Galvanometer.

v- Calculate $\frac{V_g}{I_g}$ by using the following formula

$$I_g = \frac{E}{R+R_g}$$

Step: 03: Calculation of High Resistance(R_H):-

v- High Resistance is calculated through the following formula $R_H = \frac{V}{I_g} - R_g$ where all the required values in I_g formula are already found.

v- Now connect the circuit according to figure 04. The combination of galvanometer and ~~voltmeter~~ in series act as constructed ~~galvanometer~~ while another voltmeter is connected to test the accuracy of constructed voltmeter.

v- Insert key 1 and apply resistance of R_H and note of the deflection of galvanometer in divisions.

v- Apply potential difference to the voltmeter from ~~R_H~~ for measuring v.

v- Convert the divisions of galvanometer to volts by using formula $V_g = \frac{\text{Range} \times \text{div}}{30}$.
v- Compare the values of V and V_g to find the error in the circuit.

- ii- The galvanometer and voltmeter should be with-out zero error.
- iii- Try to keep the length of high and small resistance same. to avoid resistance error.
- iv- Connect the wires and keys tight across connections to minimize probability of error
- v- Do not change galvanometer or voltmeter during an experiment.

Experiment No: 04:

To study variation of photoelectric current with intensity of Incident light.

Photoelectric Current:-

The phenomena in which electrons are released from the surface of conductor when ultraviolet light falls on it. The phenomena is known as photo electric effect and the current due to ejected electrons is photoelectric current. The light should be of particular frequency. Mathematically:-

$$I = \frac{E}{A} = \frac{E}{4\pi d^2} \Rightarrow I = K/d^2$$


So $I \propto 1/d^2$ where I is intensity of light.

Principle of Experiment:

The experiment is based on the principle of photoelectric current. When light from light source falls on surface of conductor it emits electrons from metal surface. While the microammeter connected in circuit measures the intensity of current due to emitted electrons.

Apparatus:-

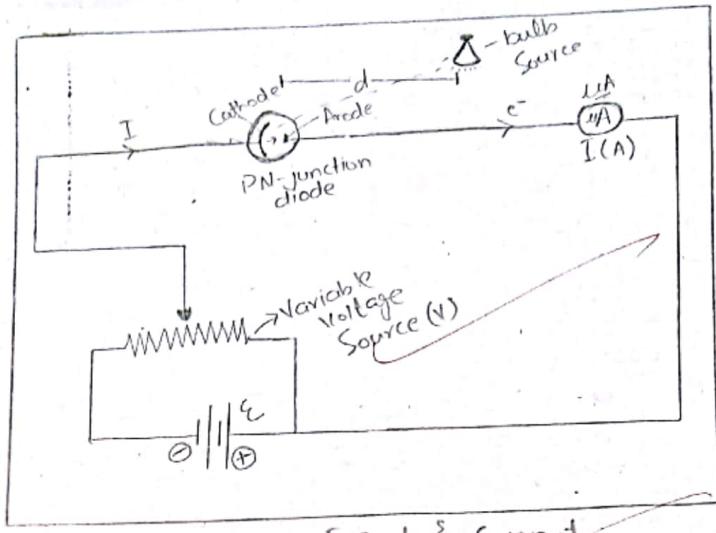- Voltmeter
- Power Supply
- Photoelectric Apparatus.
- Micrometer
- Meter Rod



Photoelectric Effect & Current

Mathematically

$$E_i \geq E_e$$

$$E_i \geq \phi \text{ (work function)}$$

$$h\nu \geq h\nu_0$$

$$\nu \geq \nu_0 \text{ (Threshold Frequency)}$$

$$E_c = \phi + KE$$

$$h\nu = h\nu_0 + KE$$

Procedure of Experiment:

- i- Light from Source fall into a metal surface at some particular distance measured by meter rod.
- ii- Electrons emitted from a metal surface due to incident beam are called photons and current produced due to photons is called photoelectric current.
- iii- The micrometer will show deflection showing current flow through the circuit.
- iv- The circuit figure shows cathode and Anode. The diode tube cathode is connected to negative terminal of battery.
- v- The microammeter is connected in series with the circuit.
- vi- If we increase or decrease distance between bulb and conductor plate the microammeter will show deflection.
- vii- The intensity of beam depends upon the distance of source from tube. i.e.,
- viii- The voltage is changed from different values and graph is plotted.

Precautions of Experiment:-

- i-Take readings of I keeping d in regular and same range to increase and decrease to increase accuracy.

d (cm)	d^2	α (mA)	$I = \frac{1}{d^2}$
----------	-------	---------------	---------------------

Given Voltage = 100V

60 cm	3600 cm^2	2	2.7×10^{-4}
55	3025	2.5	3.3×10^{-4}
50	2500	3	4×10^{-4}
45	2025	3.5	4.9×10^{-4}
40	1600	4	6.25×10^{-4}
35	1225	5	8.1×10^{-4}
30	900	6	11.1×10^{-4}
25	625	8.5	16×10^{-4}
20	400	12	25×10^{-4}
15	225	19.5	44.4×10^{-4}
10	100	50	100×10^{-4}


Given Voltage = 150V

60	3600	4 A.M.A	2.7×10^{-6}
55	3025	5 A.M.A	3.3×10^{-6}
50	2500	6.5	4.8×10^{-6}
45	2025	7.5	6.25×10^{-6}
40	1600	9.5	8.1×10^{-6}
35	1225	12	11.1×10^{-6}
30	900	15.5	16×10^{-6}
25	625	22	25×10^{-6}
20	400	32	44.4×10^{-6}
15	225	43	64×10^{-6}
10	100	55	100×10^{-6}

Given Voltage = 200V

60	3600	4 A.M.A	2.7×10^{-6}
55	3025	8	3.3×10^{-6}
50	2500	9	4.8×10^{-6}
45	2025	10	6.25×10^{-6}
40	1600	13	8.1×10^{-6}
35	1225	16	11.1×10^{-6}
30	900	22	16×10^{-6}
25	625	31.5	25×10^{-6}
20	400	55	44.4×10^{-6}
15	225	95	64×10^{-6}
10	100	140	100×10^{-6}

- 1- Do not change light source in between the experiment to keep frequency same for each reading.
- 2- Do not use galvanometer converted to ammeter because galvanometer do not give precise value of current while microammeter gives more accurate reading.
- 3- Only change the distance of source linearly. Do not change the angle of source to avoid inconsistency in current.
- 4- Do not expose the photocell to external/stay light. It can alter your readings.

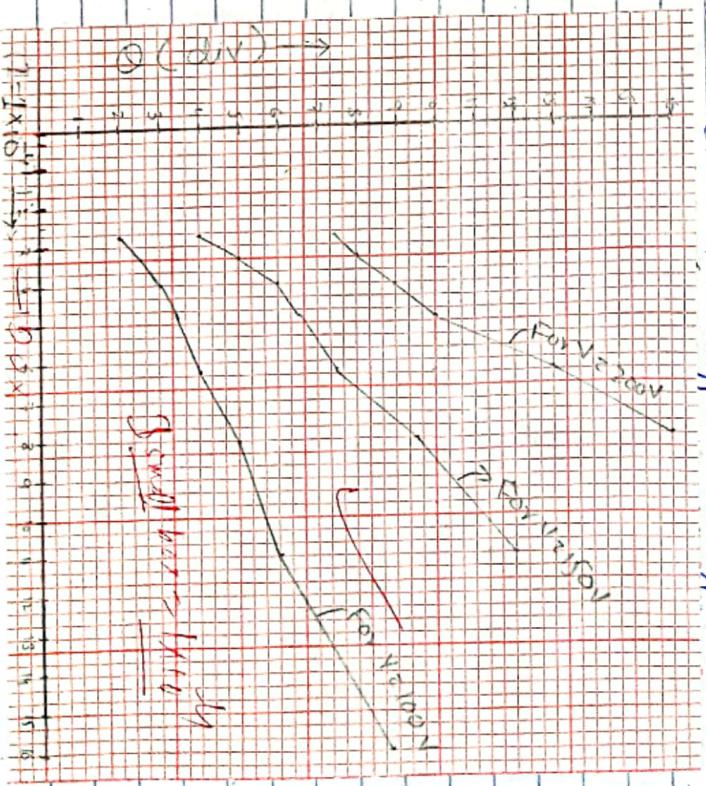

Graph of calculated values

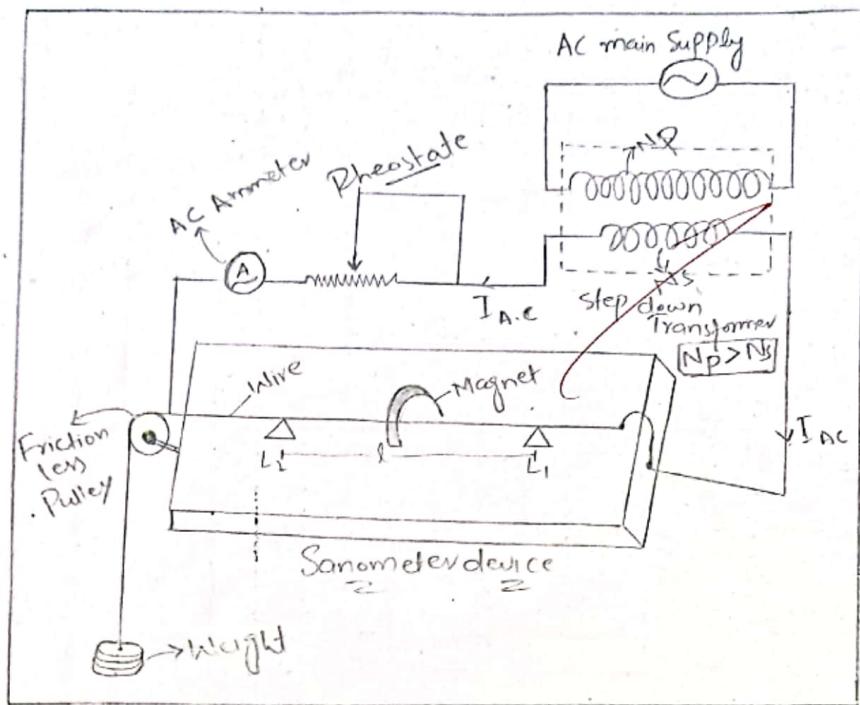


Figure of Experiment : Samometer device

$$L = \pi r^2 = \pi (2L)^2 = 4\pi L^2$$

$$V = \sqrt{\frac{4E}{\rho}} = \sqrt{\frac{I}{\rho L}} = \sqrt{\frac{I}{\mu L}}$$

where μ is linear mass density

$$V = f \lambda \Rightarrow f = \frac{V}{\lambda}$$

By putting values

$$f = \frac{1}{2L} \sqrt{\frac{I}{\mu}}$$

Mathematical equation

Experiment No: 05.

To find the frequency of A.C main by Samometer

Samometer:

It is a device used for demonstrating the relationship between the frequency of sound that is produced by the string when it is plucked and the tension, length and mass per unit length of the string. The sound is produced in transverse standing waves.

Principle of Experiment:

The experiment is based on the principle of resonance. When transverse waves are excited in a stretched wire the bridges act as a rigid reflection of these waves. Due to rigid reflection, stationary waves are formed at nodes at the bridge edges. $\lambda = \pi/2L \Rightarrow f = 1/2L \sqrt{T/\mu}$

Apparatus:-

- ↳ Samometer
- ↳ Weights
- ↳ Step down transformer
- ↳ Alternating Current (A.C) main Supply
- ↳ Ammeter
- ↳ Rheostate
- ↳ Wedges
- ↳ Magnet

For Conducting Wire: $\mu = m/L = 0.052 g/cm$

Table of Measurements

$m(g)$	T (g/cm)	L_1 (cm)	L_2 (cm)	$L_2 L_1$ (cm)	$\sqrt{T} \left(\frac{g}{cm} \right)$	$f_2 \frac{1}{2L} \sqrt{\frac{T}{\mu}}$
1000	980,000 g/cm	7 cm	50.2 cm	353.2 cm	989.94	49.9 Hz
1500	1470,000	7	62.5	55.2	1212.43	48.1
2000	1960,000	7	69.5	62.5	1450	49.11
2500	220,500	7	70	63	1684.9	52.09
2750	245000	7	75.5	68.5	1865.2	50.32
3000	2695000	7	79	72	1841.6	49.99
3500	2940000	7	81.5	76	1714.6	49.46
3750	3675000	7	90	83	1917	50.64

$$\text{Average Frequency} = \langle f \rangle = 50.07 \text{ Hz}$$


Result :- So the frequency of alternating current is approximately 50 Hz.

- Procedure of Experiment:-
- i- Arrange the Apparatus as shown in fig-
 - ii- Switch on the supply from A.C main.
 - iii- Start increasing distance between wedges L_1 & L_2 which are placed next to each other.
 - iv- At a particular point the wire has a maximum vibration which is found by moving L_1 back and forth.
 - v- L_1 is fixed while only L_2 is moved
 - vi- The frequency of this maximum vibration is found by equation $f_2 \frac{1}{2L} \sqrt{\frac{T}{\mu}}$
 - where as 'T' is tension in the string and μ is linear mass density of wire.
 - vii- The vibration is due to the fact that current carrying conductor is placed in magnetic field. Force is experienced by the conductor perpendicular to both field and current.
 - viii- As we increase the length 'L' between L_1 wedge and L_2 wedge the wire vibration gradually increases. When the vibration of wire become equal to natural frequency of wire, the wire vibration at that point increases than normal.
 - ix- At that point when frequency of Alternating

current and wire passing the current, we find frequency of wire by equation $f = \frac{1}{2} \cdot \frac{1}{L} \sqrt{\frac{T}{\mu}}$ which is the required frequency of A.C. exciting current.

Precautions of Experiment:-

(1)

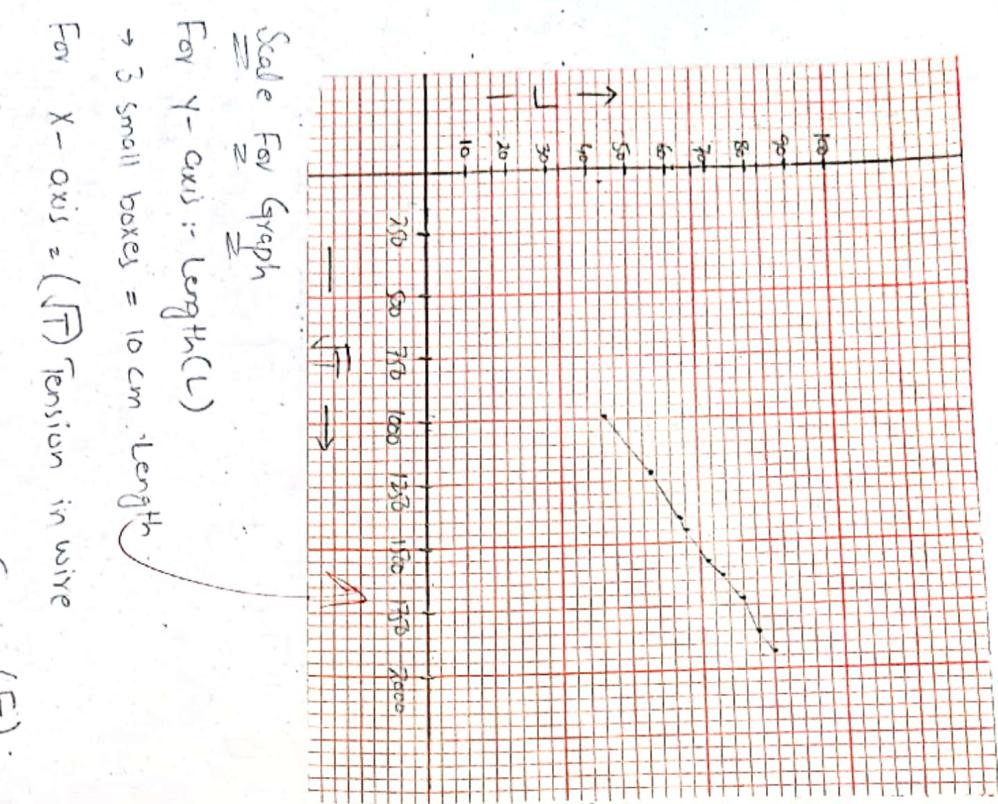

Scale for graph

For Y-axis :- length(L)

$\rightarrow 3$ small boxes = 10 cm. Length

For X-axis = (\sqrt{T}) Tension in wire

\rightarrow One small box = 50 g/cm. of tension(T)

i- keep the hanging weight straight and in rest while experimenting to avoid error in tension of string.

ii- There should be no kinks in wire or sonometer

iii- keep the pulley of sonometer frictionless.

iv- change the position of L, slowly otherwise the resonance point will be missed.

v- Find the distance b/w L & L_r at various points by changing weight and tension in wire for multiple readings.

vi- The magnet should be placed in such position so that magnetic field is perpendicular to wire.

Experiment No: 06

To determine the given high Resistance by leakage Method.

Ballistic Galvanometer:-

The Galvanometer which is used to estimate the quantity of charge flow through it is called ballistic galvanometer. It consists of moving coil which has a large moment of inertia so that it responds to the quantity of charge passed (Rather than the size of the current). It is suitable for measuring very small currents.

Apparatus:-

- ↳ Ballistic Galvanometer
- ↳ Three keys
- ↳ Cell
- ↳ Stopwatch.
- ↳ High Resistance
- ↳ Capacitor ($1\mu F = 1 \times 10^{-6} F$)

Procedure:-

1. Set the ballistic galvanometer on zero point.
2. To get reading of galvanometer deflection draw out the Damping key. So that the current should pass through ballistic galvanometer.
3. Press key 1. The capacitor will charge for

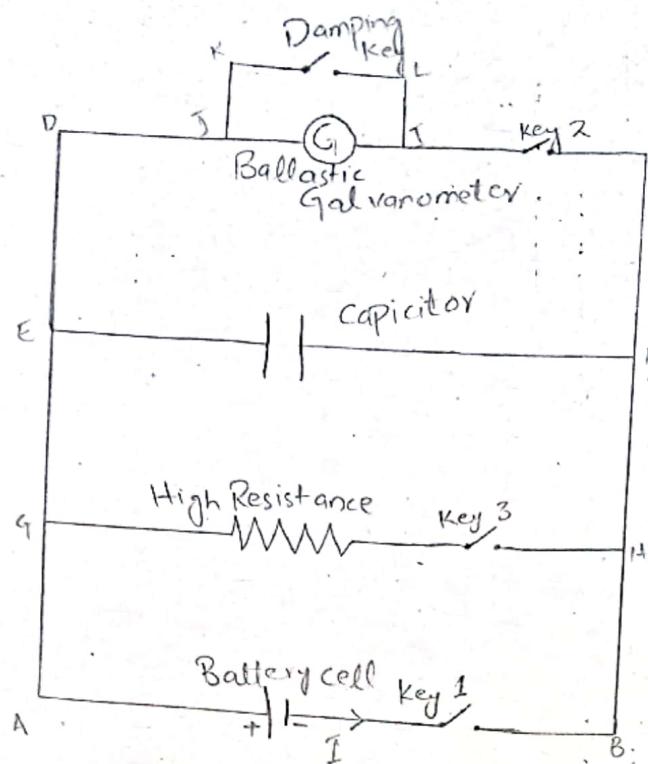


Diagram for Method of Leakage

Table For Experiment

SNo	θ_0	$t(s)$	θ_t	$R = \frac{t}{C \ln(\frac{\theta_0}{\theta_t})} \text{ (2)}$
1	78	3.22	59	$11.5 \times 10^6 \Omega$
2	79	4.2	53	$10.5 \times 10^6 \Omega$
3	67	2.7	59	$10.6 \times 10^6 \Omega$
4	78	2.92	58	$9.1 \times 10^6 \Omega$
5	74	2.84	57	$10.8 \times 10^6 \Omega$
6	72	2.47	58	$11.4 \times 10^6 \Omega$
7	78	2.99	57	$9.5 \times 10^6 \Omega$

So the Average Resistance

$$\langle R \rangle = \frac{10.4 \times 10^6 \Omega}{7}$$

at θ_t

x- This deflection will be less than θ_0 because some charge is already been leaked by pressing key 3 and remaining by key 2 again.

x- Use of the formula $R_2 = \frac{t}{C \ln(\frac{\theta_0}{\theta_t})}$

to find the value of resistance where 'C' is the capacitance of capacitor whose value is $1 \times 10^{-6} F$. (1 UF).

Precautions of Experiment:

1- The galvanometer coil should be free

Sometime Then release key 1.
x- Now press key 2. The charge will peak
capacitor to galvanometer and hence it will
show reading.

v- Note the deflection θ_0, θ_0 for the first
or highest deflection of pointer (light spot)
x- Now put the damping key again and
charge the capacitor by pressing key 1.
v- Now release key 1 and press key 3.
for a known time 't'. Note the time 't'
and release key 3.

v- Now Again press key 2, the galvanometer
will show deflection again. Note the reading
at θ_t .

x- This deflection will be less than θ_0
because some charge is already been
leaked by pressing key 3 and remaining
by key 2 again.

to rotate.

"- Damping key should be pressed when the spot is coming crossing zero of the circle. Scale.

"- Both the lower terminals of high resistance are to be connected.
iv- Charge the capicitor before taking reading of O-

(A)

9/11

13/11/27